

Arrow Vision Series

WEBENCH[®] Power Designer

Power Supply Design In Seconds!

Objectives



WEBENCH® Overview



Efficiency Calculation and Design Optimization



Electrical and Thermal Simulation



Build it and Reporting

13 Years of Modeling and Verification

Faster & More Effective

Offline Past



Trial and Error

1999 Online




WEBENCH®
Design Tools

2009 Visualizer



2010 FPGA
Power Architect

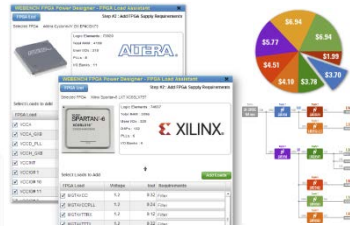

Agile Systems

2012 FPGA System
Power Architect



Complete Systems

New Capabilities

WEBENCH[®] Tools

Power Designer

Power supply and system power architecture

LED Designer

LED driver design and LED architecture

Sensor Designer

Sensor analog front end design

Active Filter Designer

Filter design and simulation

PLL Designer

PLL implementation

Amplifier Designer

Op amp design and simulation

Beginning to end: Design and Prototyping

1. Choose a Part




Enter Specifications




Select Part

2. Create a Design

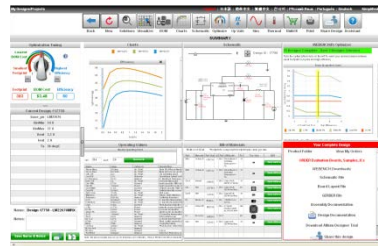


Optimize for Footprint and Efficiency, Use Graphs to Visualize Design

3. Analyze a Design

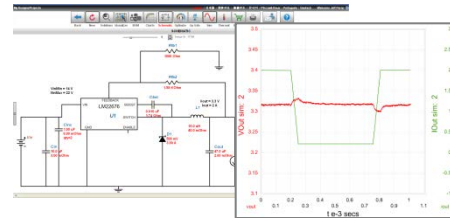


Generate Schematic/
Electrical Analysis

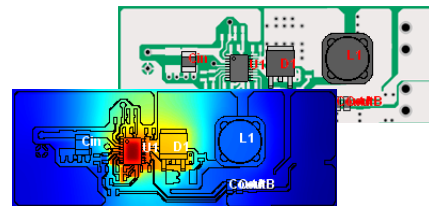

Generate Layout/
Thermal Analysis


4. Build It!

Schematic Export
Custom Prototype Kit

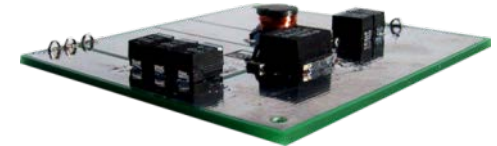

Prototype

The WEBENCH[®] Power Tool Suite

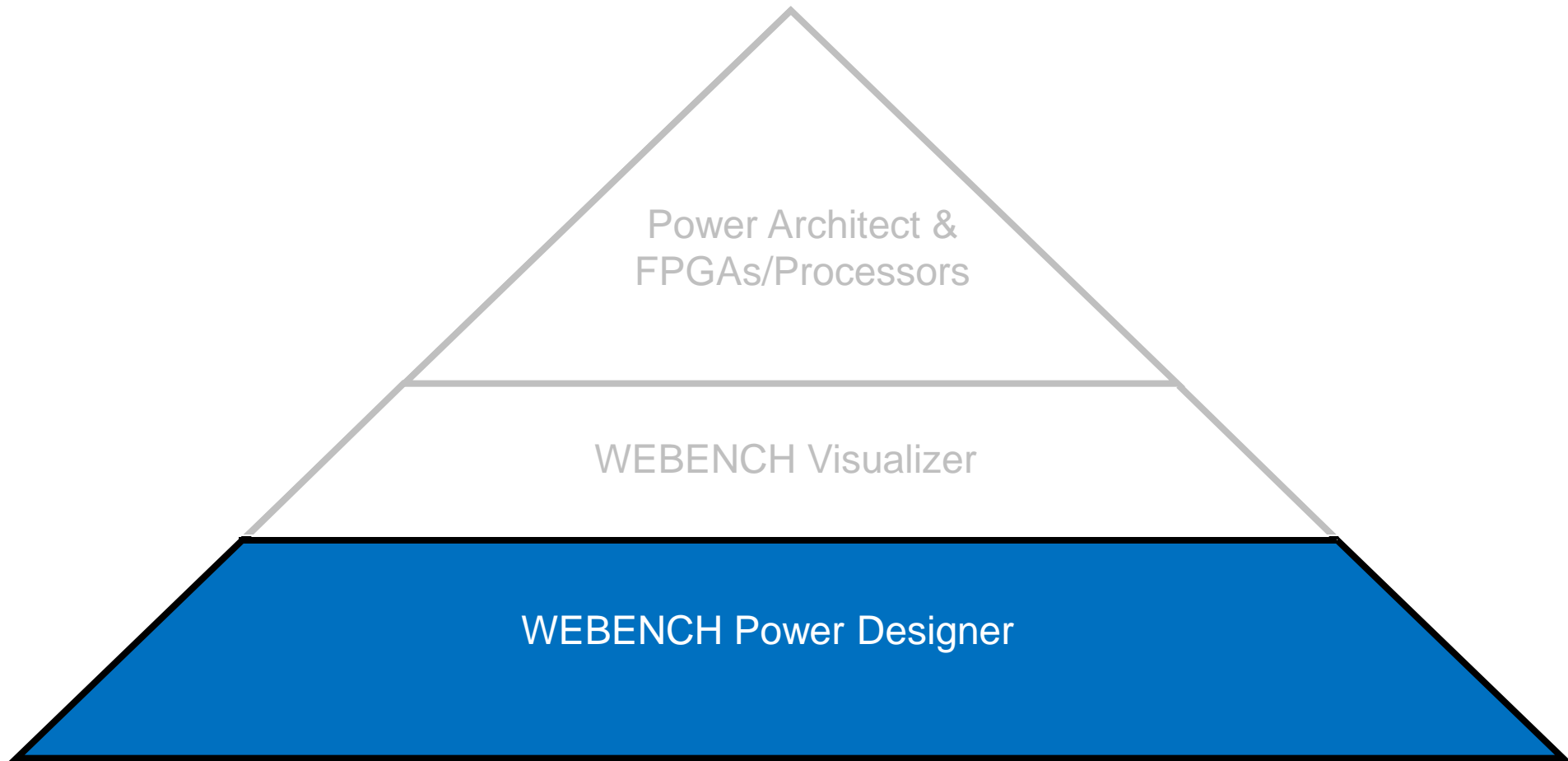

WEBENCH® Supports Broad Portfolio

13 Years of Modeling and Verification

Circuit Calc & Sim model

- LM10500
- LM2012x/3x/4x/54
- LM20242
- LM20323/33/43
- LM21212/5
- LM21305
- LM(2)5005/07/10/11
- LM(2)5085/88
- LM(2)5085/88
- LM(2)5116
- LM(2)5117
- LM26001/3
- LM2696
- LM2734/35/36
- LM27341/2
- LM27341/2
- LM2734/5/6
- LM27402
- LM2743
- LM2830/31/32
- LM2841/42
- LM2852/53/54
- LM3100/02/03
- LM3478/88/81
- LM34910/17/19/23/30
- LM3670/71/73/74
- LM5001/02/6/8/9
- LM5022
- LMR10510/15/20
- LMR12010
- LMR14203/6
- LMR24210/20
- LMR62421
- LMZ22008/10
- TPS2420
- TPS92550/1

Circuit Calc but no Sim model

- LM(2)5118/9
- LM2622
- LM3224
- LM2700
- LM2698
- LM2731
- LM3668
- LMR62010/4
- TPS40170
- TPS40210
- TPS40303/4/5
- TPS51225
- TPS51315
- TPS53313/6
- TPS5401
- TPS54040
- TPS54060/61/62
- TPS5410/20/30/50
- TPS54140/60
- TPS54218
- TPS54231/2/3
- TPS54240/60
- TPS54310-8
- TPS54320/5/6
- TPS54331/2
- TPS54418
- TPS54478
- TPS54610-8
- TPS61170/5
- TPS62080/1/2
- TPS62125
- TPS62130/1/2/3
- TPS62140/1/2/3
- TPS62150/1/2/3
- TPS62200-8
- TPS62240/2/3
- TPS622601/2/3
- TPS62290/1/3
- TPS842/4/610


WebTHERM /Build It

- LM22671-9, LM22680
- LM(2)5574/5/6
- LM2585/6/7/8
- LM2595/6/8/9
- LM2670-9
- LM3150/1/2/3
- LM3402/4(HV)
- LMZ10503/4/5
- LMZ12001/2/3/8/10
- LMZ13608/10
- LMZ14201/2/3
- LMZ22003/5/8/10
- LMZ23603/5

Switchers/Controllers/LED Drivers:
378 base part numbers
LDOS: 50 base part numbers

Supported Topologies: Buck (over 60% of total designs), Boost, Flyback, SEPIC, Inverting Buck/Boost, LDO, HotSwap, Modules

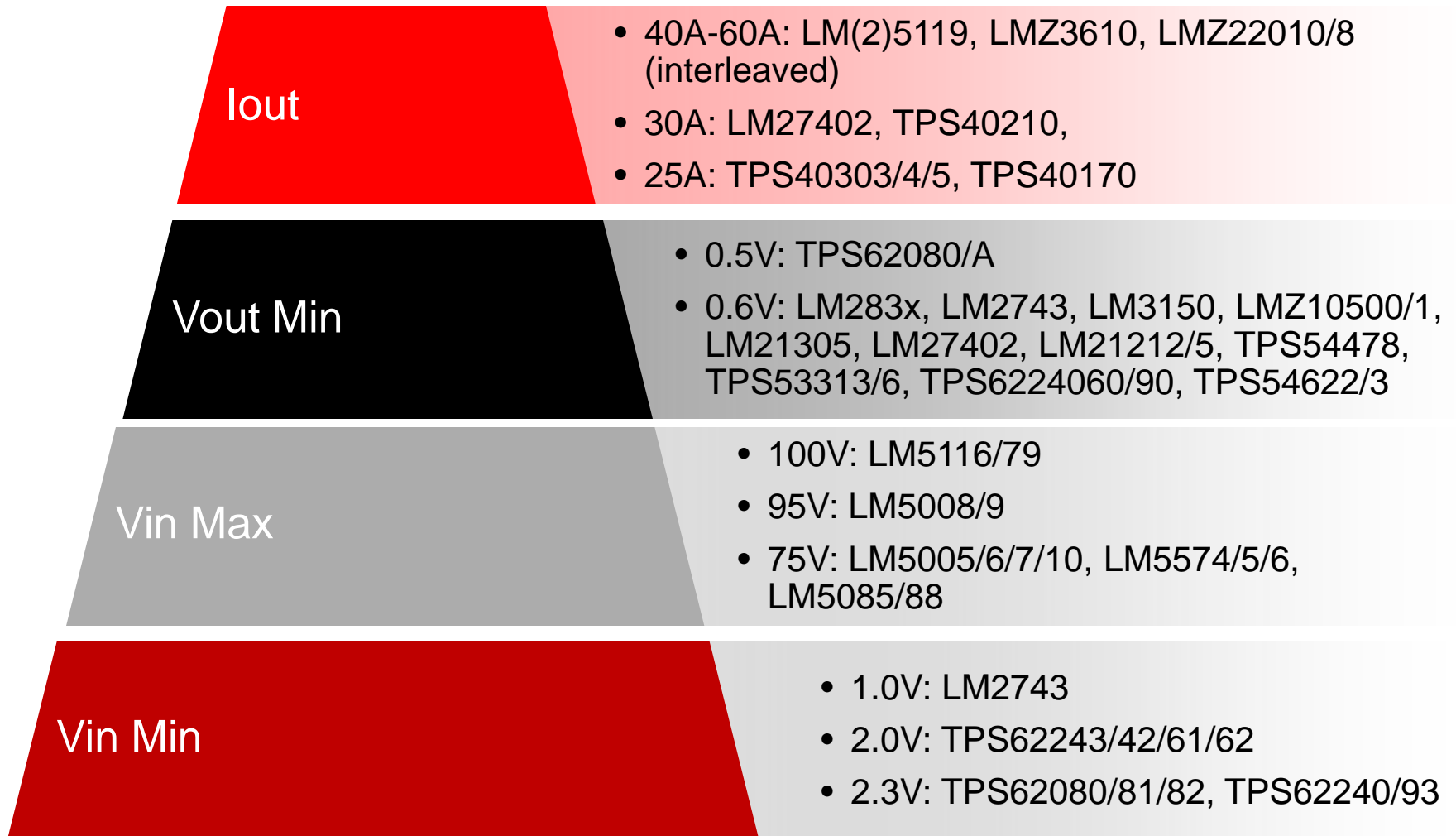Coverage of WEBENCH® enabled parts (Buck Switchers)



Multilingual Capability

Select from the language bar

Japanese,
Chinese,
Korean,
Russian,
Portuguese,
German


The screenshot displays the TI WEBENCH Visualizer interface. At the top, a language bar is highlighted with a red box and an arrow, showing options: English, 日本語, 简体中文, 繁體中文, 한국어, Русский Язык, Português, and Deutsch. Below this, the interface is divided into several sections:

- Top Bar:** My Designs/Projects, English | 日本語 | 简体中文 | 繁體中文 | 한국어 | Русский Язык | Português | Deutsch, Welcome jeff.perry@ti.com
- Navigation:** New, Solutions, Visualizer, Assistant
- Visualizer Section:**
 - Language Bar:** English | 日本語 | 简体中文 | 繁體中文 | 한국어 | Русский Язык | Português | Deutsch
 - Controls:** Smallest Footprint, Highest Efficiency, Footprint (208), BOM Cost (\$3.61), Efficiency (80%), Recalculate
 - Parameters:** Vin Max: 22V, Vout: 3.3V, Iout: 2A, Amb. Temp: 30°C, Show Alternate Topologies, Show Only Modules
 - Options:** On/Off Pin, Adj Lpk Lim, Error Pin, Adj Frequency, Soft Start, Sync Switching, Ext Sync, Controller, Module, Integrated Switch, LDO
 - Performance Metrics:** Footprint: 208mm², 935mm², Frequency: 150kHz, 1000kHz, BOM Cost: \$0, \$21, Crossover: 0kHz, 82kHz, BOM Count: 5, 33, Phase: 0°, 103°, Margin
- Advanced Charting:** X Axis: Efficiency, Y Axis: Footprint, Bubble Size: BOM Cost. A bubble chart shows various solutions, with a callout for 'Smallest & Most Efficient'.
- Solutions Table:** Solutions: (70 found) Show All Columns. The table lists parts, their BOM images, design considerations, and performance metrics.

Part	Create	WEBENCH® Tools	Schematic	BOM Images	Design Considerations	BOM Footprint (mm²)	BOM Cost	Eff (%)	BOM Count	Fr (kHz)
LMR24220	Open Design			208mm²	High Efficiency	208	\$3.61	80%	11	60
LM3151-3.3	Open Design			478mm²	SIMPLE SWITCHER(r) Controller	478	\$3.62	92%	12	24
LM2676-3.3	Open Design			565mm²	Third Generation SIMPLE SWITCHER	565	\$2.95	83%	9	26

Arrow WEBENCH Designer

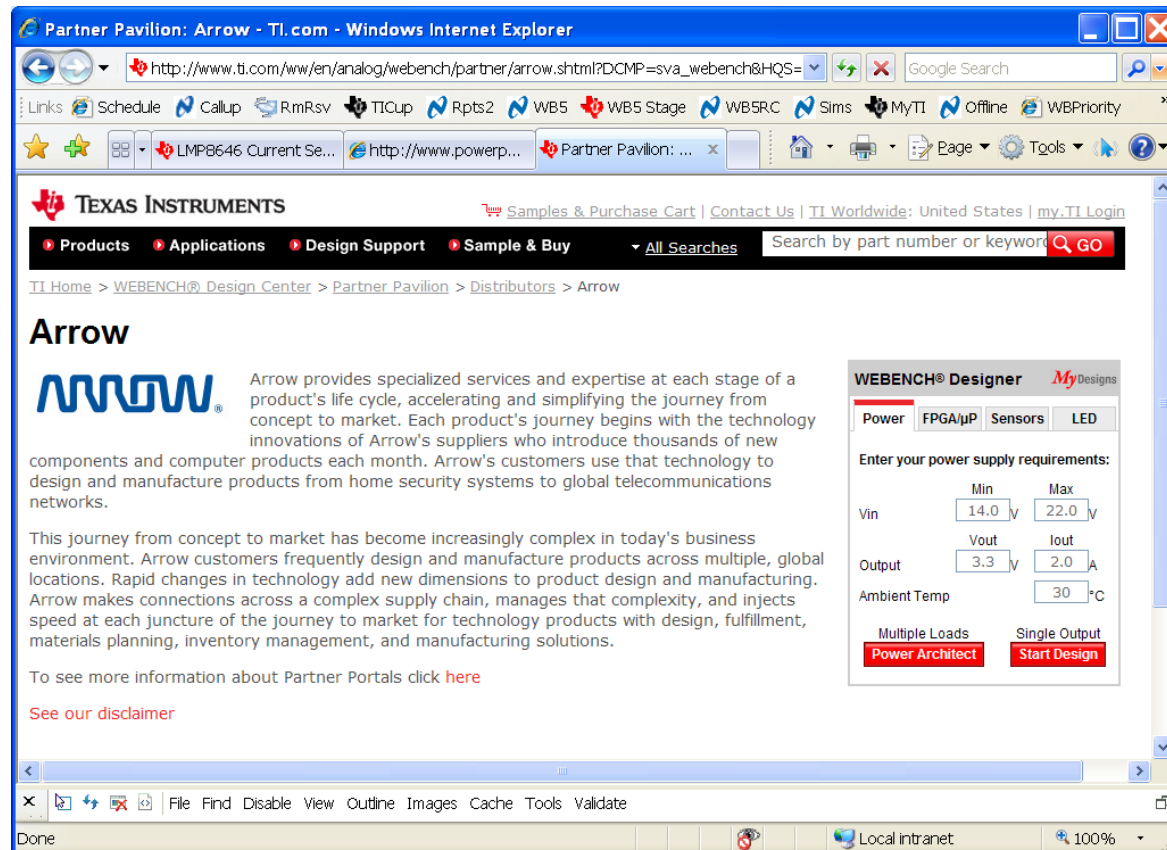- Access customized versions of WEBENCH® Designer:
- <http://ti.com/arrow>



Ways to Access WEBENCH® Designer

The screenshot shows the Texas Instruments website with the WEBENCH® Designer interface. The top navigation bar includes links for Products, Applications, Tools & Software, Support & Community, Sample & Buy, and About TI. A search bar is also present. The main content area features a sidebar with product categories and a central panel for the WEBENCH® Designer. The designer panel has tabs for Power, FPGA/μP, Sensors, and LED. The Power tab is selected, showing a form to enter power supply requirements. The form includes input fields for Vin (Min 14.0 V, Max 22.0 V), Vout (3.3 V), Iout (2.0 A), and Ambient Temp (30 °C). Below the form are two buttons: Power Architect and Start Design.

TEXAS INSTRUMENTS

Sample & Purchase Cart | English | 简体中文 | 日本語 | my.TI Login

Products Applications Tools & Software Support & Community Sample & Buy About TI Search

WEBENCH® System Power Architect

Advanced design tool for power management including hot-swap controllers

Start your design today for free

WEBENCH® Designer

Power FPGA/μP Sensors LED

Enter your power supply requirements:

	Min	Max	
Vin	14.0 V	22.0 V	
Vout	3.3 V	Iout	2.0 A
Ambient Temp	30 °C		

Multiple Loads Single Output

Power Architect Start Design

Browse products

- Amplifiers & Linear
- Audio
- Broadband RF/IF & Digital Radio
- Clocks & Timers
- Data Converters
- DLP® & MEMS
- High-Reliability
- Interface
- Logic
- DLP® - TV, Projectors, & Cinema

- Power Management
- Processors
 - ARM® Processors
 - Digital Signal Processors
 - Microcontrollers (MCU)
 - OMAP™ Applications
- Switches & Multiplexers
- Temperature Sensors & Wireless Connectivity
- Calculators & Education

View new products

- Use the entry panel on:
<http://www.ti.com>
- Select the specific tool
 - Power
 - Power Architect
 - Start Design
 - FPGA/μP
 - Sensors
 - LED

Ways to Access WEBENCH® Designer

TEXAS INSTRUMENTS

Products Applications Design Support Sample & Buy

Search by part number or keyword **GO**

TI Home > Semiconductors > Power Management > Switching Regulator > DC/DC Converter (Integrated Switch) > Step-Down Regulator >

LM22672
(ACTIVE) 1A SIMPLE SWITCHER®, Step-Down Voltage Regulator with Features

No reviews yet. [Add your review and give us feedback.](#)

Description & Features Sample & Buy Technical Documents Tools & Software Support & Community

Datasheet


 **LM22672/2Q 42V, 1A SIMPLE SWITCHER Step-Down Regulator with Features (Rev. K)**
(PDF, 447 KB) 08 Jun 2012

[View All Technical Documents](#)

See Also

- > **LM22670** - 3A, Features Adjustable Switching Frequency Or Frequency Sync Up To 1MHz And Precision Enable
 - > **LM22671** - 0.5A Version
 - > **LM22673** - 3A, Features Adjustable Soft-Start And Adjustable Current Limit
- [View All](#)

Diagrams (3)

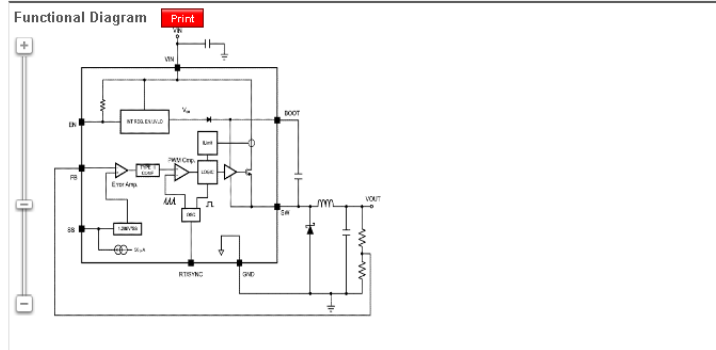

Featured Tools and Software

- > **LM22671 1A SIMPLE SWITCHER Regulator w/ Freq Adj or Synch and Precision Enable EVM** (Evaluation Modules & Boards)
 - > **LM2267x, LM22680 Quick Start Simple Switcher Component Calculator** (Calculation Tools)
 - > **Power Stage Designer of Most Commonly Used Switchmode Power Supplies** (Circuit Design & Simulation)
- [View All](#)


WEBENCH® LM22672

	Min	Max	Range
Vin	11.00	13.00 V	4.50 – 42.00V
Vout	5.00	V	1.28 – 37.00V
Iout	1.00	A	≤ 1.00A
Ambient Temp	30	°C	≤ 100°C

Lowest BOM Cost | Smallest Footprint | Highest Efficiency

Footprint: 207 | BOM Cost: \$2.43 | Efficiency: 87%

[Open Design](#)

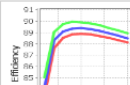

OR

- Go to the product folder for a specific part
- Enter your specifications

WEBENCH® Navigation

Navigation Icons

WEBENCH Tools:

Power

LED

LED Architect

Power Architect

FPGA / Processor

Power Architect

HotSwap

The screenshot displays the WEBENCH navigation interface. At the top, there are four icons: a red circular arrow labeled 'New', a magnifying glass labeled 'Solutions', a grid with a cursor labeled 'Visualizer', and a question mark labeled 'Assistant'. Below these is a tabbed interface with tabs for 'Power', 'LED', 'LED Architect', 'Power Architect', 'FPGA/µP', and 'HotSwap'. The 'Power' tab is selected, showing a 'Basic Selection' section with input fields for Vin Min (14 V), Vin Max (22 V), Vout 1 (3.3 V), Iout 1 (2 A), and Op Ambient Temp (30 °C). Below this is a 'Choose Additional Features (Optional)' section with checkboxes for 'Show Alternate Topologies' and 'Show Only Modules', and radio buttons for 'On/Off Pin', 'Error Flag', and 'Sync Pin' (all set to 'Ignore'). Further down are input fields for Vout 2 (0 V), Iout 2 (0 A), Vout 3 (0 V), and Iout 3 (0 A). A 'Coupon Code' field is also present. A green button labeled 'Show Recommended Power Management ICs' is at the bottom, followed by a 'Show All: ?' link and three red links: 'Switching Regulators', 'Linear Regulators', and 'Switched-Capacitors'.

From webench.ti.com, Find All Parts Supported by WEBENCH Power Designer

Products

TI Home > WEBENCH® D

WEBENCH

WEBENCH Designer
sensing applications
before a design is co

WEBENCH

Get results fa
that deliver d

Start your de

WEBENCH® Ar

- > Power Architect (m
- > System Power Arch
- > Processor Power A
- > FPGA Power Archi
- > LED Architect (ente
- > All WEBENCH Too

WEBENCH® De

- > Power (single, multi
- > Power Designer Parts Listing
- > LED (enter LED)

WEBENCH® Power Designer Enabled Devices

Switchers LDO Hotswap

TPS6170

TPS61175

TPS62080

TPS62080A

TPS62081

TPS62082

42 / 527 item(s)

Reset


Create		WEBENCH Tools	Topology	Design Consideration
		<input type="checkbox"/> Circuit Calculator <input type="checkbox"/> Thermal Simulation <input type="checkbox"/> Electrical Simulation <input type="checkbox"/> Build It	Filter...	
		Open Design	Boost	High Voltage Boost Converter
2	TPS61175	Open Design	Boost	3A High Voltage Boost Controller with :
3	TPS62080	Open Design	Buck	1.2A High Efficient Step Down Converte
4	TPS62080A	Open Design	Buck	1.2A High Efficient Step Down Converte
5	TPS62081	Open Design	Buck	1.2A High Efficient Step Down Converte
6	TPS62082	Open Design	Buck	1.2A High Efficient Step Down Converte
7	TPS62125	Open Design	Buck	3V-17V, 300mA Buck Converter With Av
8	TPS62130	Open Design	Buck	3V-17V, 3A, DCS-Control, pin selectab
9	TPS62131	Open Design	Buck	3V-17V, 1.8Vout, 3A, DCS-Control, pin se
10	TPS62132	Open Design	Buck	3V-17V, 3.3Vout, 3A, DCS-Control, pin se
11	TPS62133	Open Design	Buck	3V-17V, 5Vout, 3A, DCS-Control, pin sele

Export to Excel

Export to CSV

- ☒ Index
- ☒ Part
- ☒ Create
- ☒ WEBENCH Tools
- ☒ Topology
- ☐ On/Off
- ☐ Err Pin
- ☐ Soft Start
- ☐ Ext Sync
- ☐ Adj Ipk
- ☐ Adj Freq
- ☐ Sync Switching
- ☐ Controller
- ☐ Vin Min (V)
- ☐ Vin Max (V)
- ☐ Vout Min (V)
- ☐ Vout Max (V)
- ☐ Iout Max (A)
- ☐ Min Freq
- ☐ Max Freq

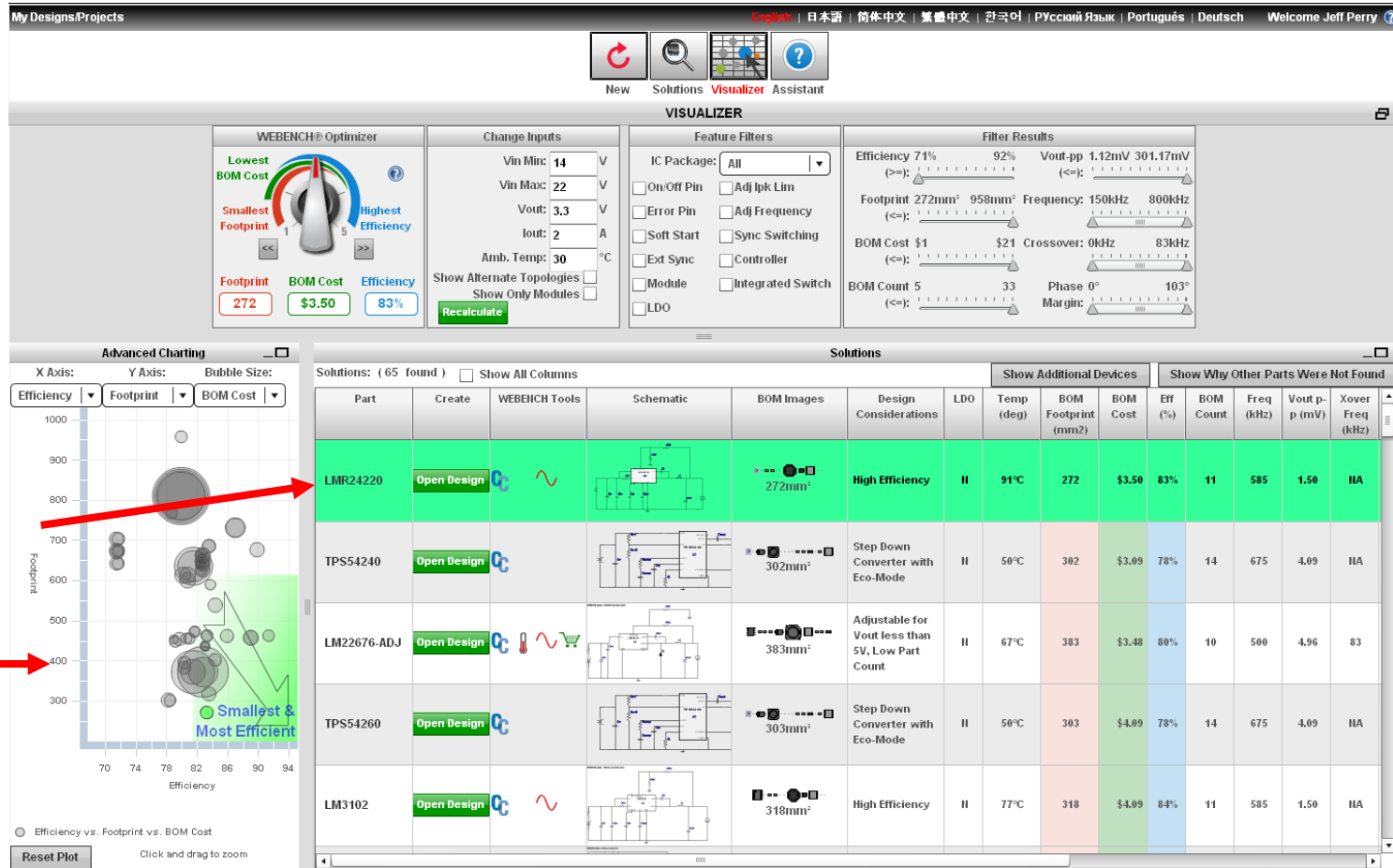WEBENCH® Visualizer- Calculates 65 Designs in Seconds




Create and View Design

Simulation

Dashboard

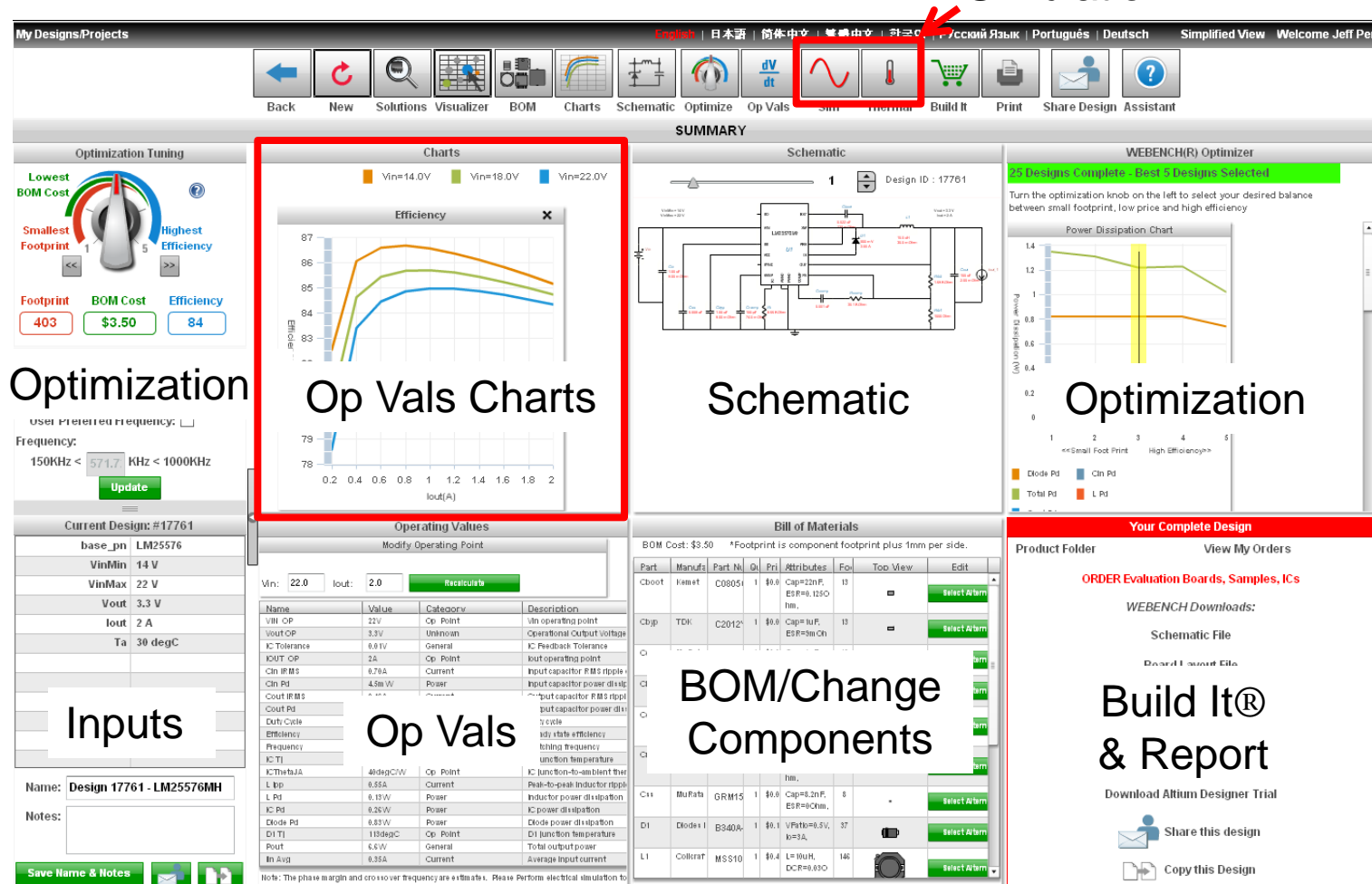- 1) Graphs
- 2) Schematic
- 3) Optimization
- 4) Operating values
- 5) BOM
- 6) Reporting



Schematic – Buck Converter

Components:

Input Capacitor

Regulator with integrated FET


Inductor

Catch Diode

Output Capacitor

Feedback Network


Feature Controls

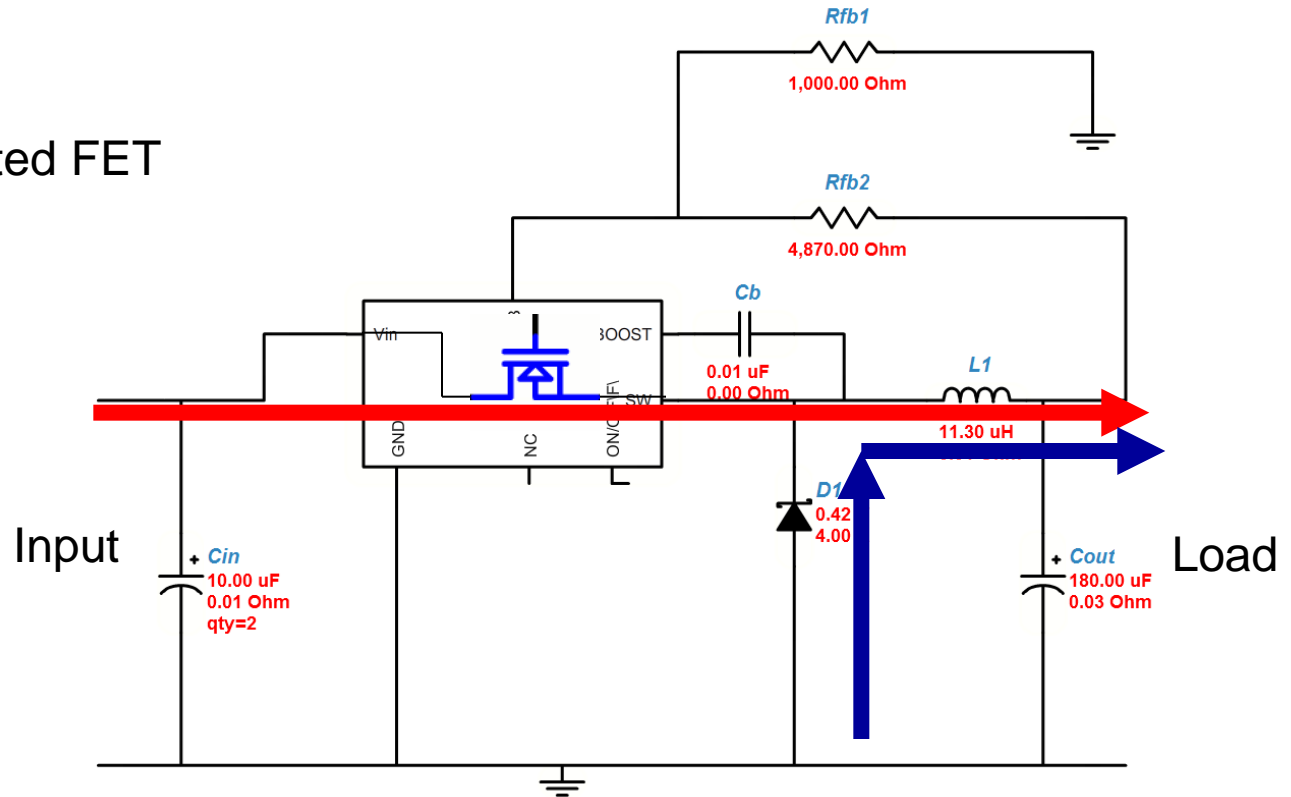

Current Path with Switch On


Current Path with Switch Off

Visualize Behavior – Power Dissipation

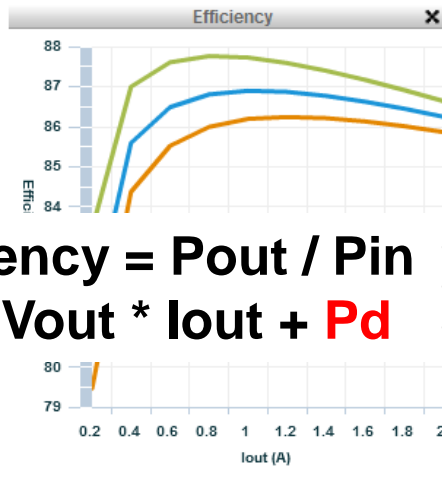

$$\text{Efficiency} = P_{\text{out}} / P_{\text{in}}$$

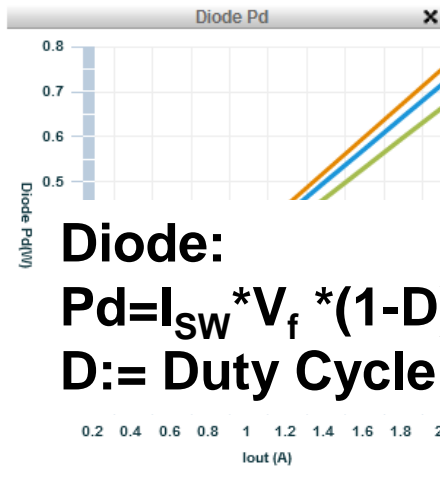
$$P_{\text{in}} = V_{\text{out}} * I_{\text{out}} + P_d$$



Diode:

$$P_d = I_{\text{SW}} * V_f * (1-D)$$

D := Duty Cycle

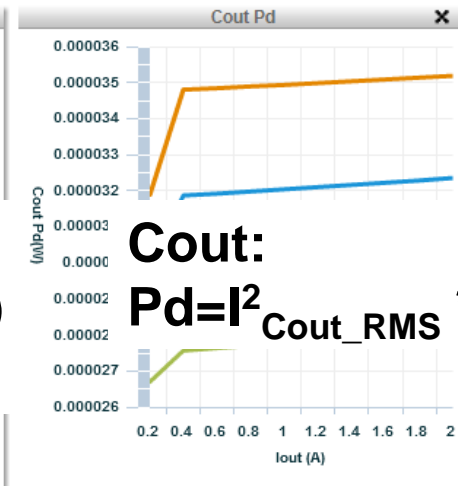

Cout:

$$P_d = I_{\text{Cout_RMS}}^2 * \text{ESR}$$




Regulator:

$$P_{d_{\text{DC}}} = I_{\text{SW_RMS}}^2 * R_{\text{DS-ON}} * D$$


$$P_{d_{\text{AC}}} = \frac{1}{2} * V_{\text{in}} * I_{\text{SW}} * (T_{\text{rise}} + T_{\text{fall}}) * f_{\text{SW}}$$
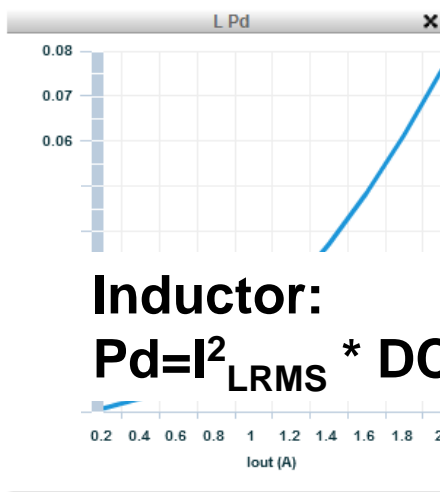
$$P_{d_{\text{Quiescent}}} = I_q * V_{\text{in}}$$



Inductor:

$$P_d = I_{\text{LRMS}}^2 * \text{DCR}$$

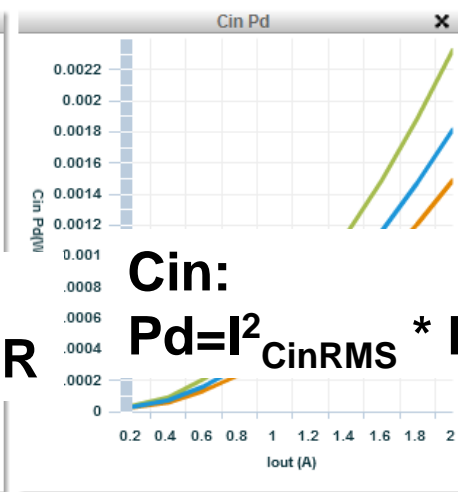


Cin:

$$P_d = I_{\text{CinRMS}}^2 * \text{ESR}$$

FET Selection: AC Loss

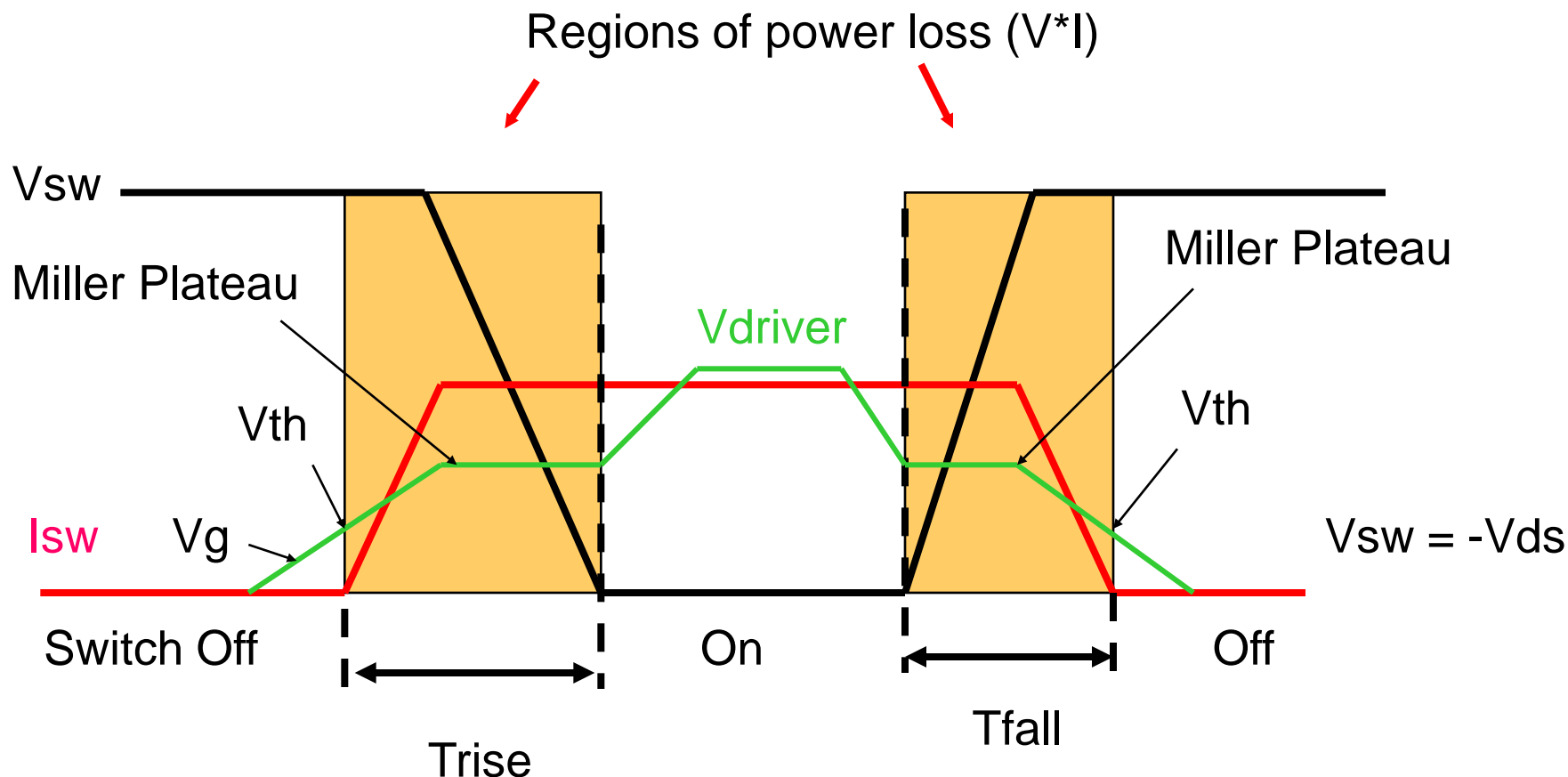- $P_{swAC} = \frac{1}{2} * V_{ds_{off}} * I_{ds_{on}} * (t_{rise} + t_{fall}) / T_{sw}$




FET Selection: AC Loss

- $P_{swAC} = \frac{1}{2} * V_{ds_{off}} * I_{ds_{on}} * (trise + tfall)/T_{sw}$

High Freq = High Loss

Low Freq = Low Loss

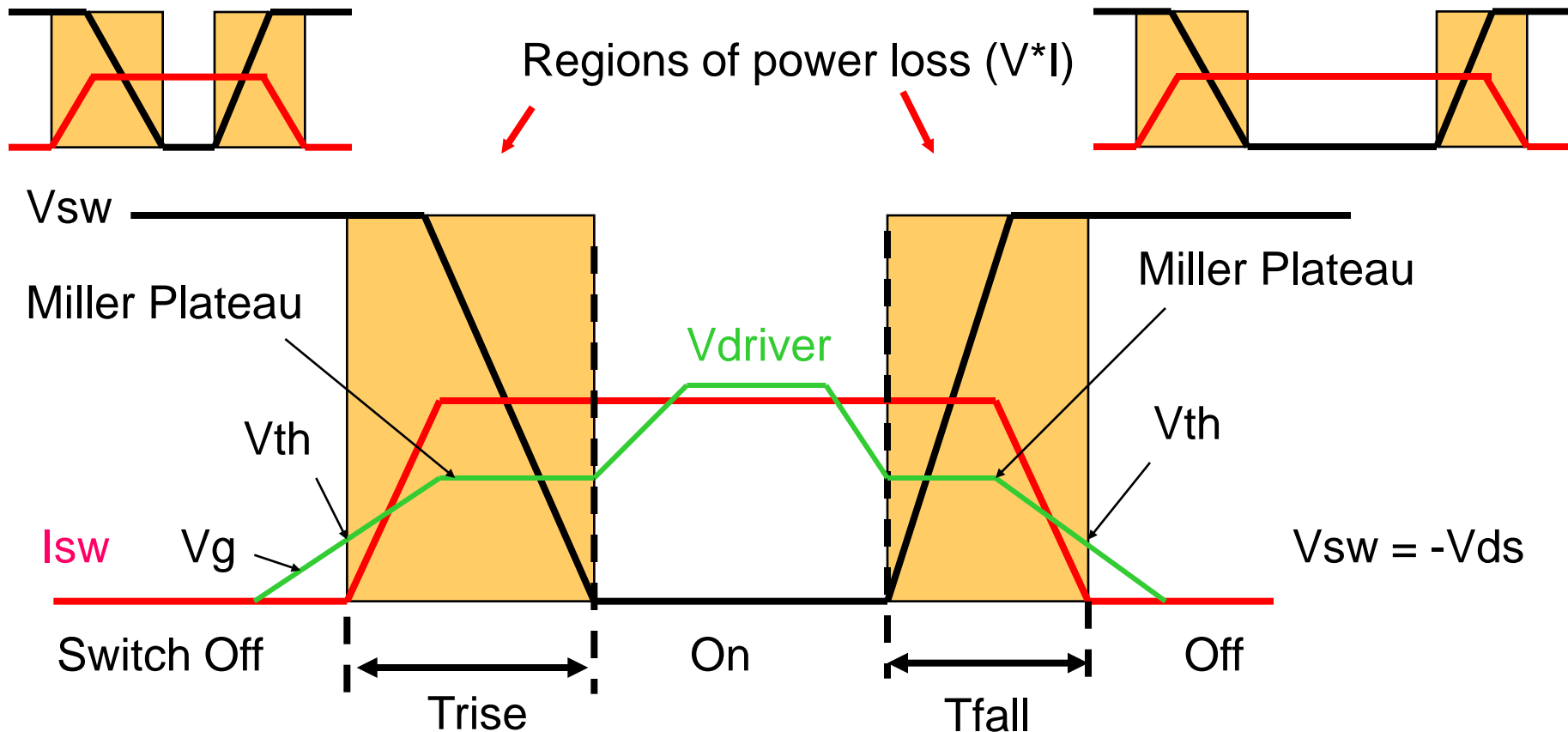


How to Reduce FET Power Loss

- **DC losses: Choose a FET with low R_{dsOn}**
- **AC losses: Choose a FET with low gate charge**
- **AC losses: Lower the switching frequency**



BUT

- **Lowering frequency affects the inductor selection**
- **We want to keep the inductor ripple current constant**
 - **Because this changes the peak switch current and the V_{out} ripple**

Inductor Current vs. Switch Voltage

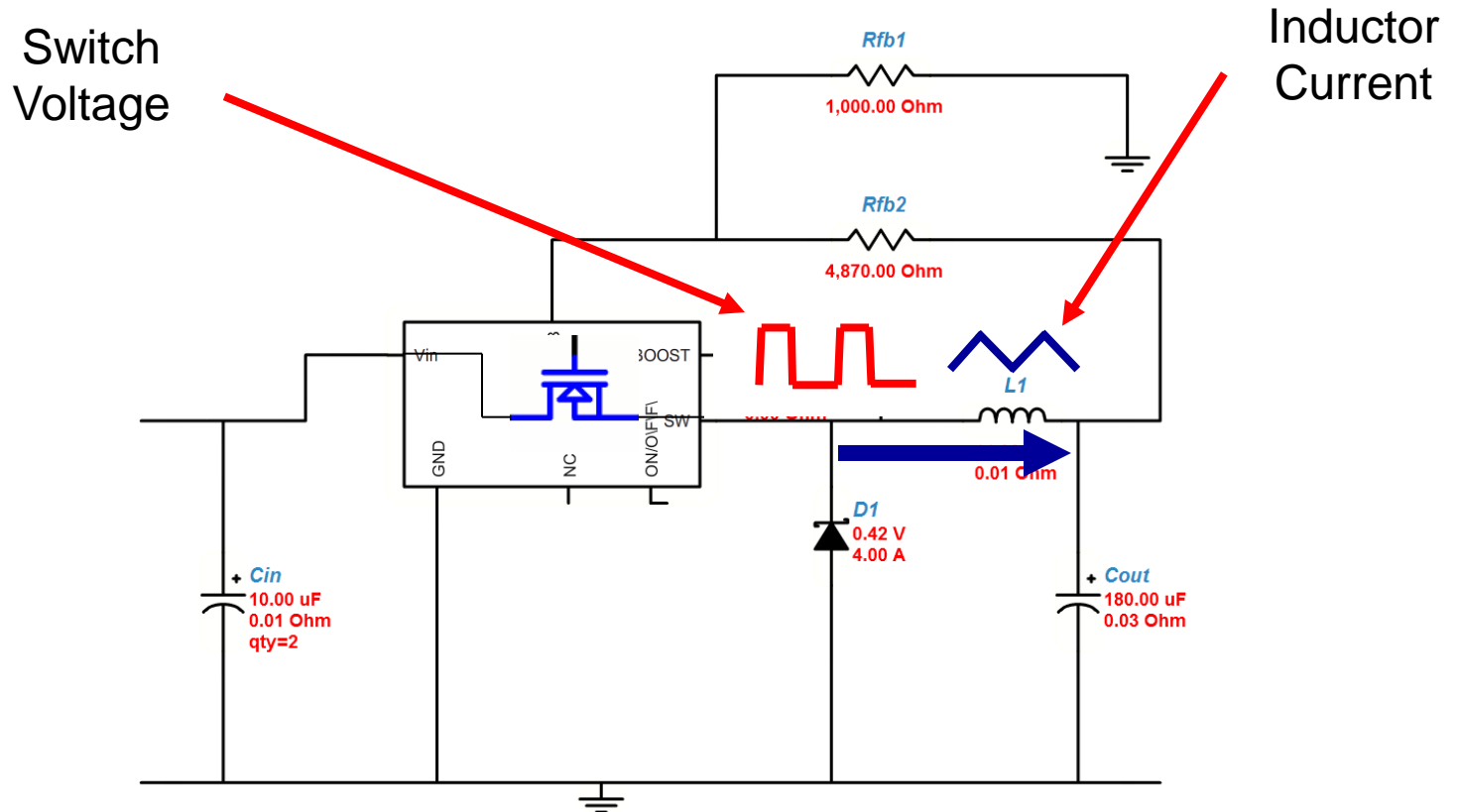

Inductor Ripple Current

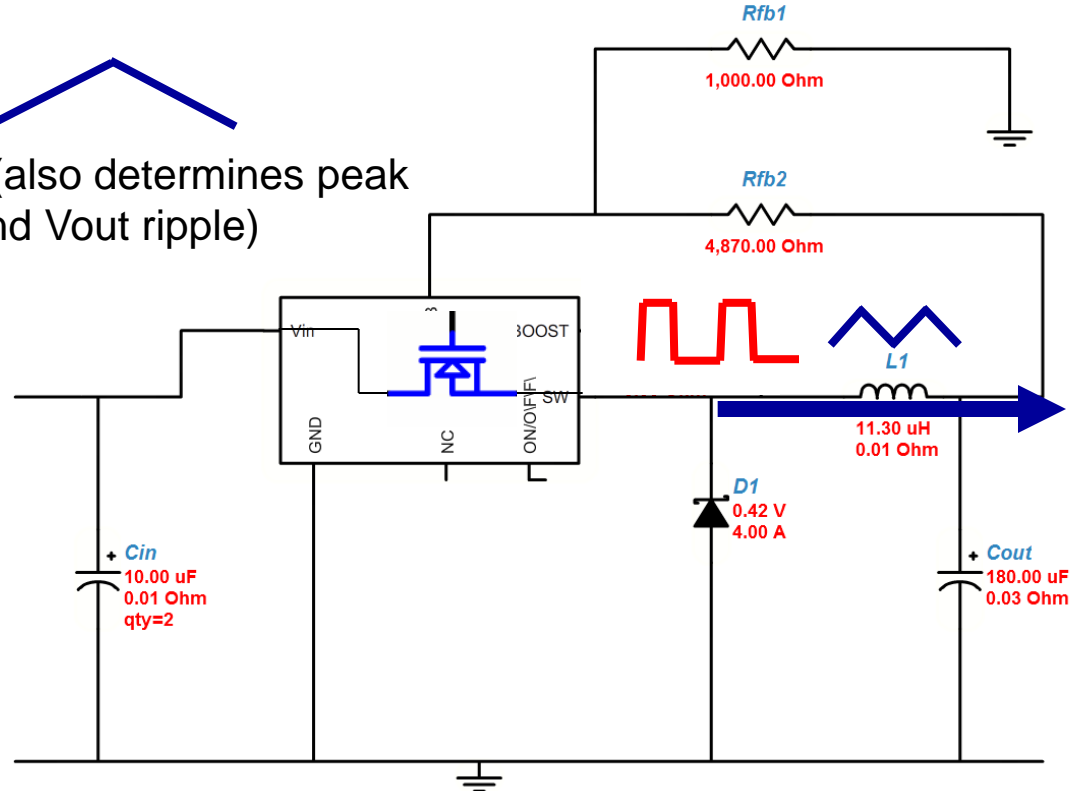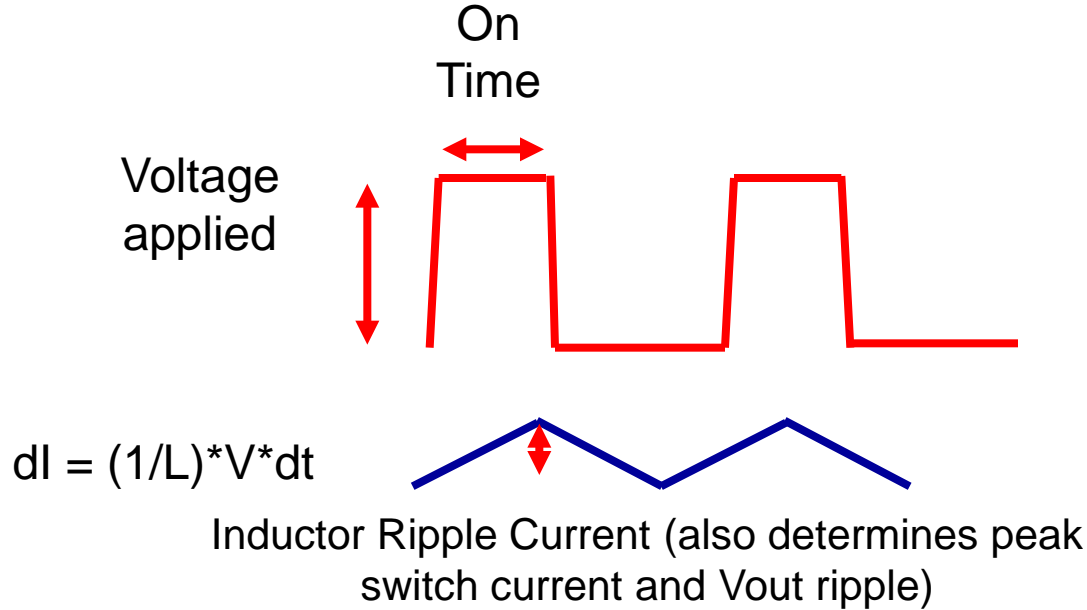


Inductor Selection – Lower Frequency

Higher frequency:

On
Time

Voltage
applied

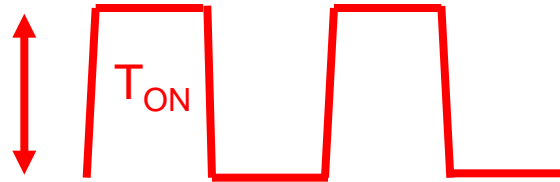


$$dI = (1/L) * V * dt$$




Inductor Ripple Current (also determines peak
switch current and Vout ripple)

Lower frequency:

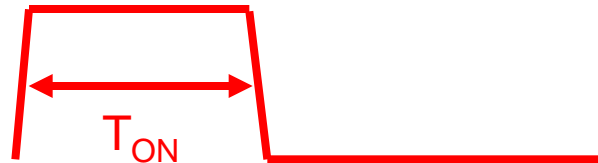


If L is kept
constant, I_{Lpp}
increases

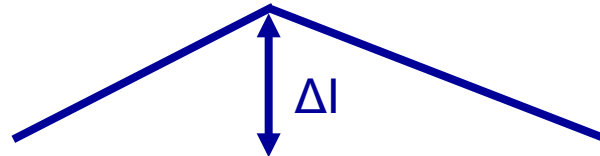

Lower Frequency =
Increased On Time =
Increased Inductor Ripple
Current =
Increased Peak Switch
Current and Increased Vout
Ripple


Inductor Selection – Raise Inductance

Higher frequency:

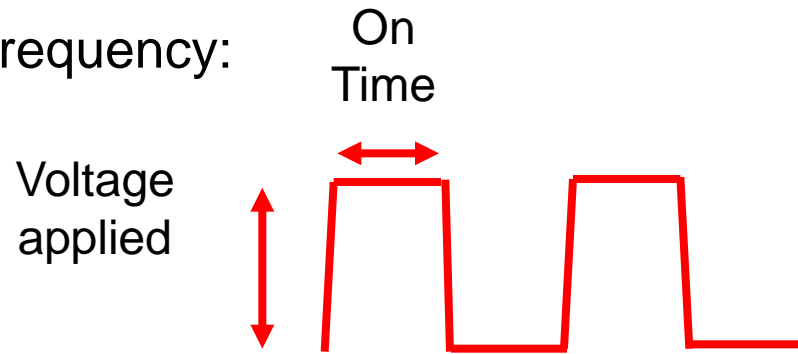


$$dI = (1/L) * V * dt$$

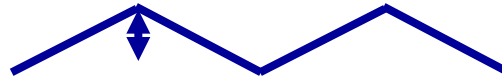Inductor Ripple Current (also determines peak switch current and Vout ripple)




Lower frequency:

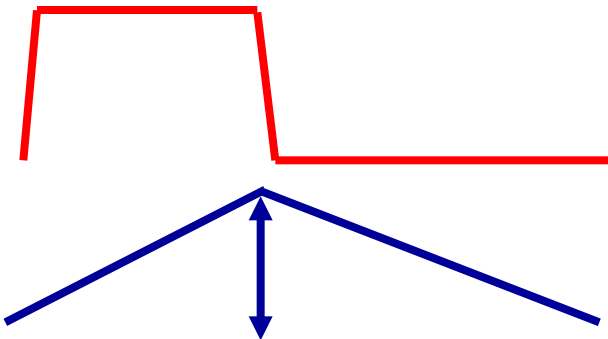

If L is kept constant, I_{Lpp} increases


Lower frequency with higher inductance:

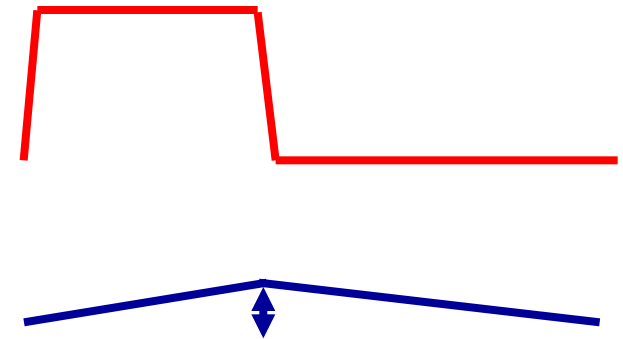

So we need to increase L

Effect of Lower Frequency on Inductor

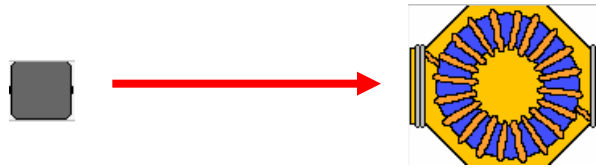- If we keep the inductor ripple current constant by increasing the inductance:
 - The inductor gets larger (more turns)
 - The inductor power dissipation goes up (longer wire)



WEBENCH® Optimizer Dial

“Dial In Your Solution”

WEBENCH® Design Optimization



Optimization Setting	Frequency	Component Selection	Summary
1 – Smallest footprint	Highest	<ul style="list-style-type: none"> • Smallest footprint • Don't care about cost 	Smallest size but lowest efficiency
2 – Lowest cost	High	<ul style="list-style-type: none"> • Lowest cost 	High frequency means smaller / cheaper components
3 – Balanced	Medium	<ul style="list-style-type: none"> • In stock • Low cost 	Balanced approach using IC's middle frequency
4 – High efficiency	Low	<ul style="list-style-type: none"> • Low DCR, ESR, Vf • Low cost 	Higher efficiency, with low cost but larger parts
5 – Highest efficiency	Lowest	<ul style="list-style-type: none"> • Low DCR, ESR, Vf • Don't care about cost 	Highest efficiency but largest parts


Key Optimization Parameters Graphed



25 Designs Complete - Best 5 Designs Selected

Turn the optimization knob on the left to select your desired balance between small footprint, low price and high efficiency

Optimize page

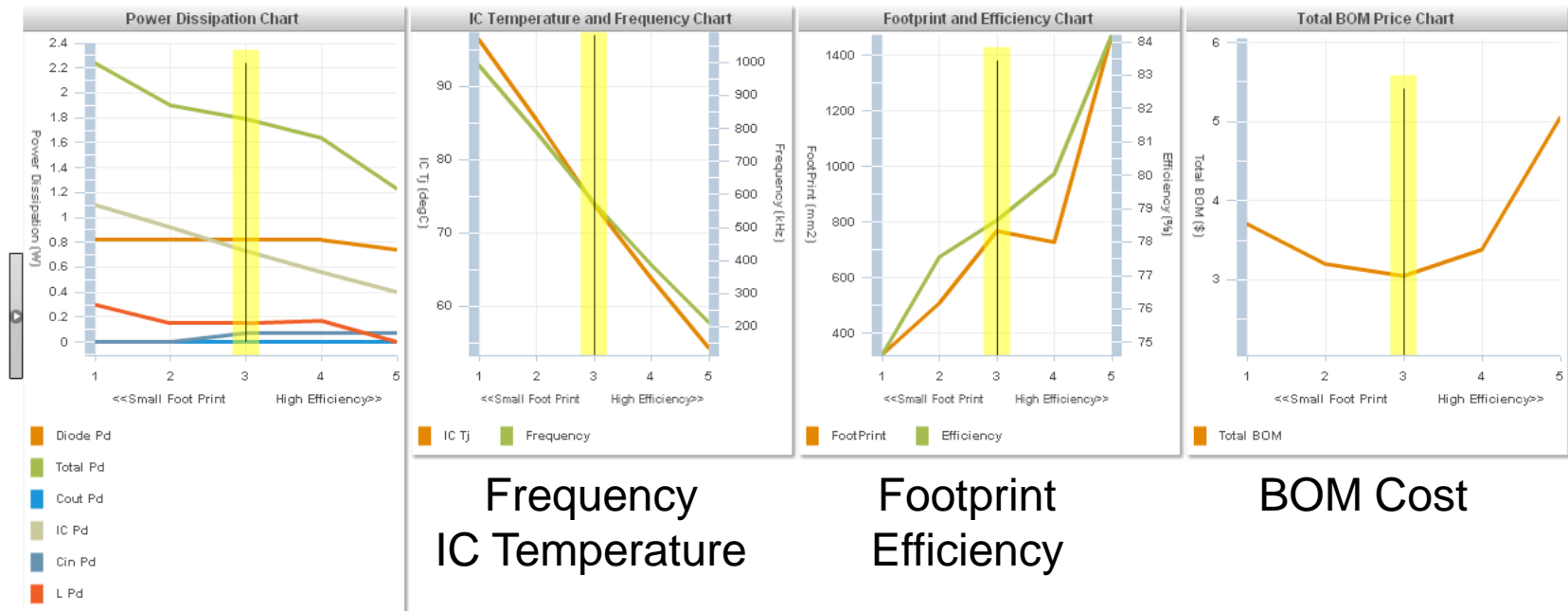

Power Dissipation
by Component


Frequency
IC Temperature

Footprint
Efficiency


BOM Cost

WEBENCH[®] Efficiency Verification


TPS54320: Vin(min,max)=8V, Vout=3.3V

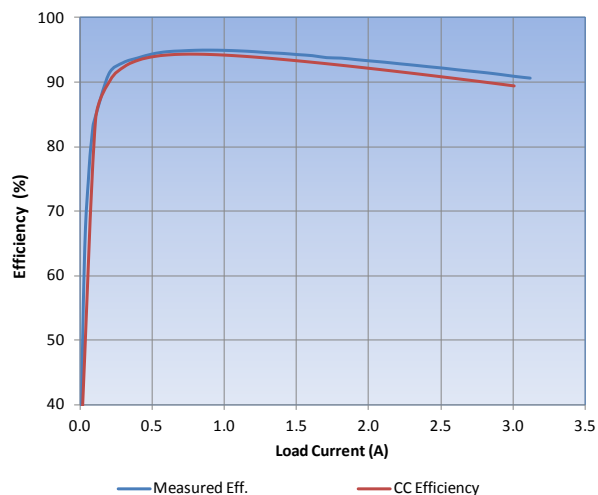


TPS54320: Vin(min,max)=12V, Vout=3.3V

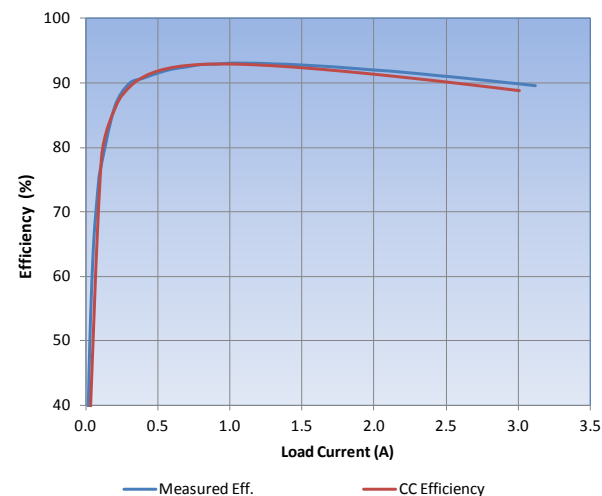

TPS54320: Vin(min,max)=17V, Vout=3.3V

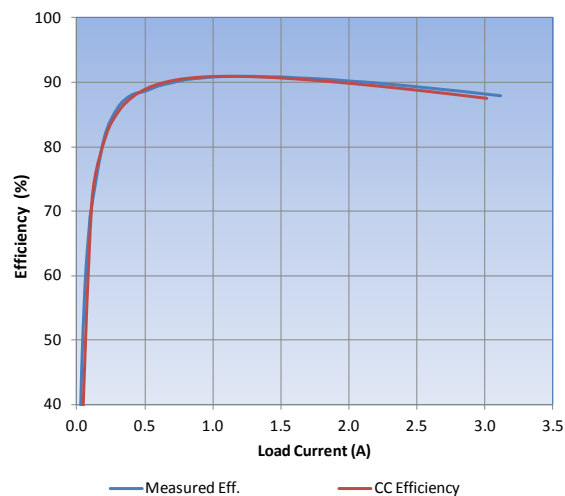

WEBENCH[®] Efficiency Verification

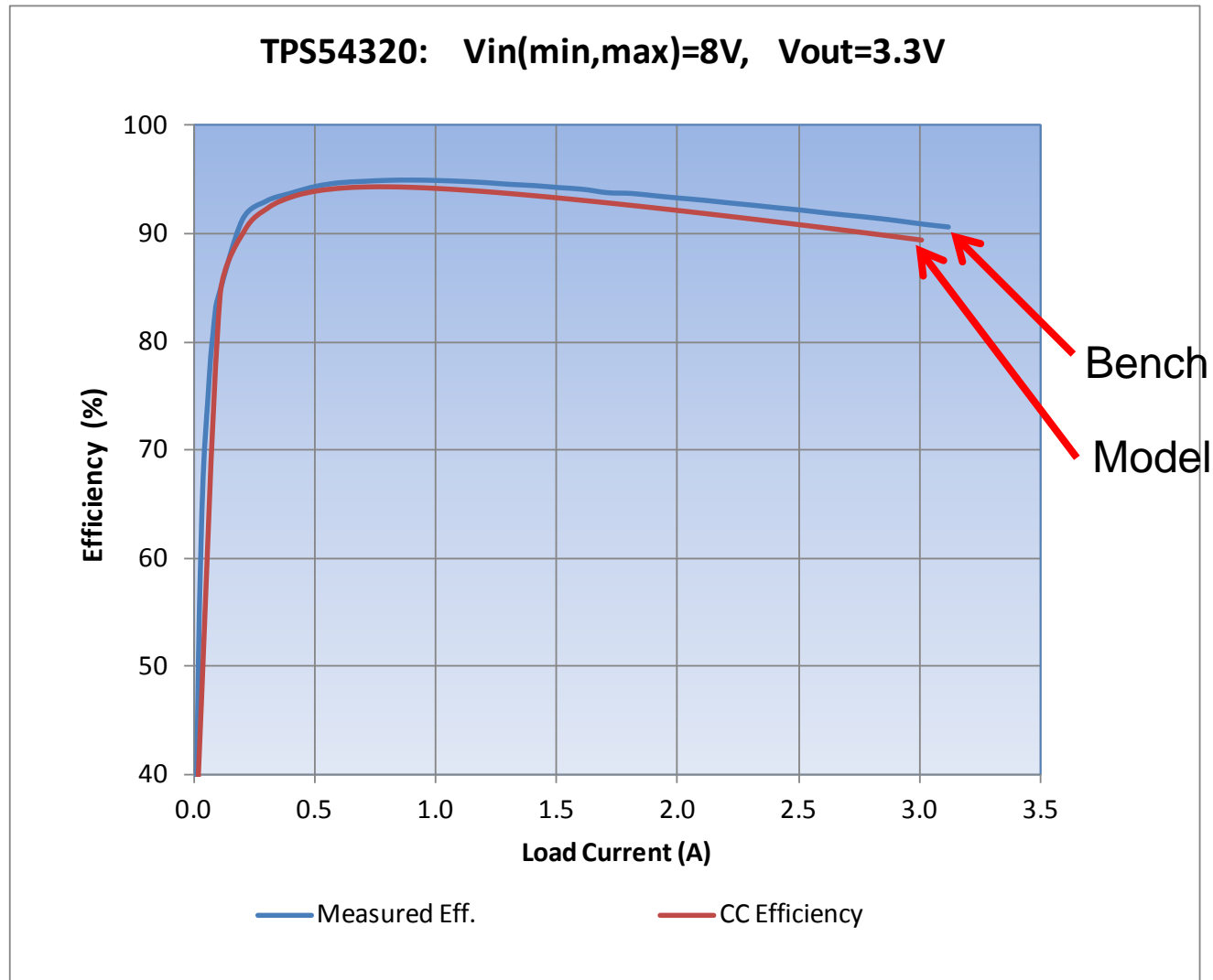

Continue to Improve Your Design: View and Change Your Bill of Materials

Click Select Alternate To Change A Component

BILL OF MATERIALS

Export to: ☒ Excel BOM Cost: \$3.50 *Footprint is component footprint plus 1mm per side.

Part	Manufacturer	Part Number	Quantity	Price	Attributes	Footprint	Top View	Edit
Cb	MuRata	GRM155R71E333	1	\$0.01	Cap=33nF, ESR=00hm, VDC=25V	8	-	Select Alternate Part
Cbyp	TDK	C2012Y5V1E1052	1	\$0.01	Cap=1uF, ESR=9m0hm, VDC=25V	13	-	Select Alternate Part
Cin	TDK	C5750X7R1H1061	1	\$0.68	Cap=10uF, ESR=3m0hm, VDC=50V	60	-	Select Alternate Part
Cinx	Kemet	C0805C104K5RA	1	\$0.01	Cap=100nF, ESR=0.0640hm, VDC=50V	13	-	Select Alternate Part
Cout	TDK	C3225X5R054501	1	\$0.39	Cap=100uF, ESR=2m0hm, VDC=25V	23	-	Select Alternate Part
Css	MuRata	GRM155R71E123	1	\$0.01	Cap=12nF, ESR=00hm, VDC=25V	8	-	Select Alternate Part
L1	Bourns	SRU8043-6R8Y	1	\$0.36	L=6.8uH, DCR=0.0220hm, IDC=3.8A	100	-	Select Alternate Part
Rfb1	Vishay-Dale	CRCW0402976RF	1	\$0.01	Resistance=9760hm, Tolerance=1%, Power=0.063W	8	-	Select Alternate Part
Rfb2	Vishay-Dale	CRCW04023K09F	1	\$0.01	Resistance=3.09K0hm, Tolerance=1%, Power=0.063W	8	-	Select Alternate Part
Ron	Vishay-Dale	CRCW040246K4F	1	\$0.01	Resistance=46.4K0hm, Tolerance=1%, Power=0.063W	8	-	Select Alternate Part
U1	Texas Instrument	LMR24220TL	1	\$2.00		25	-	

Advanced Options

Soft Start Time (ms):
1ms < 1 ms < 10ms
User Preferred Frequency: ☐
Frequency:
100KHz < 585.2 KHz < 1000KHz

Current Design: #1523

base_pn	LMR24220
VinMin	14 V
VinMax	22 V
Vout	3.3 V
Iout	2 A
Ta	30 degC


Name: Design 1523 - LMR24220TL
Notes:

Evaluate and Select Alternate Components


Parameter
Specification
Limits

Multiple
Column Sort

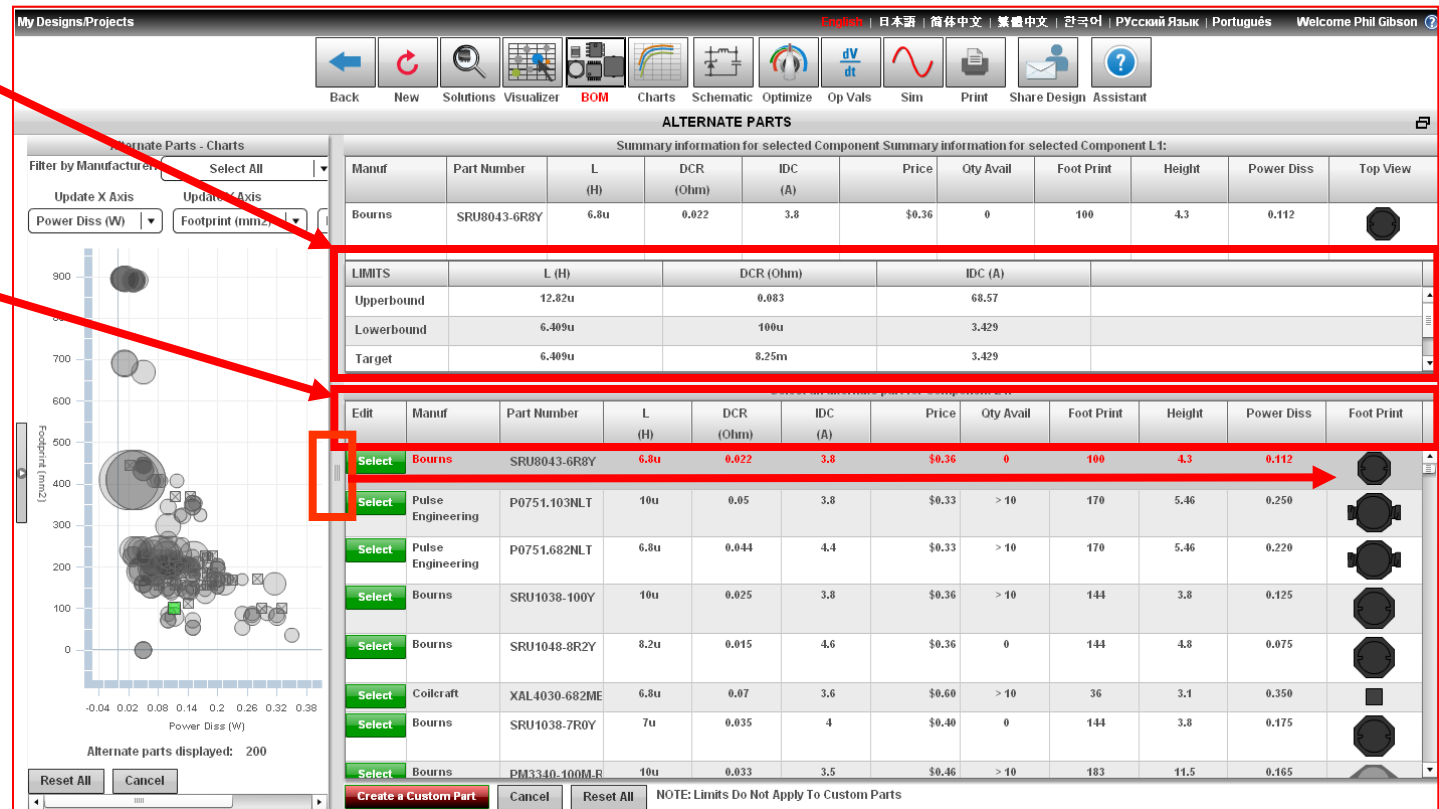
Component
Tradeoffs:
Footprint
Pdiss
Price
Performance
Vout Ripple
Transient Resp
Loop Stability




Evaluate Components - Inductor

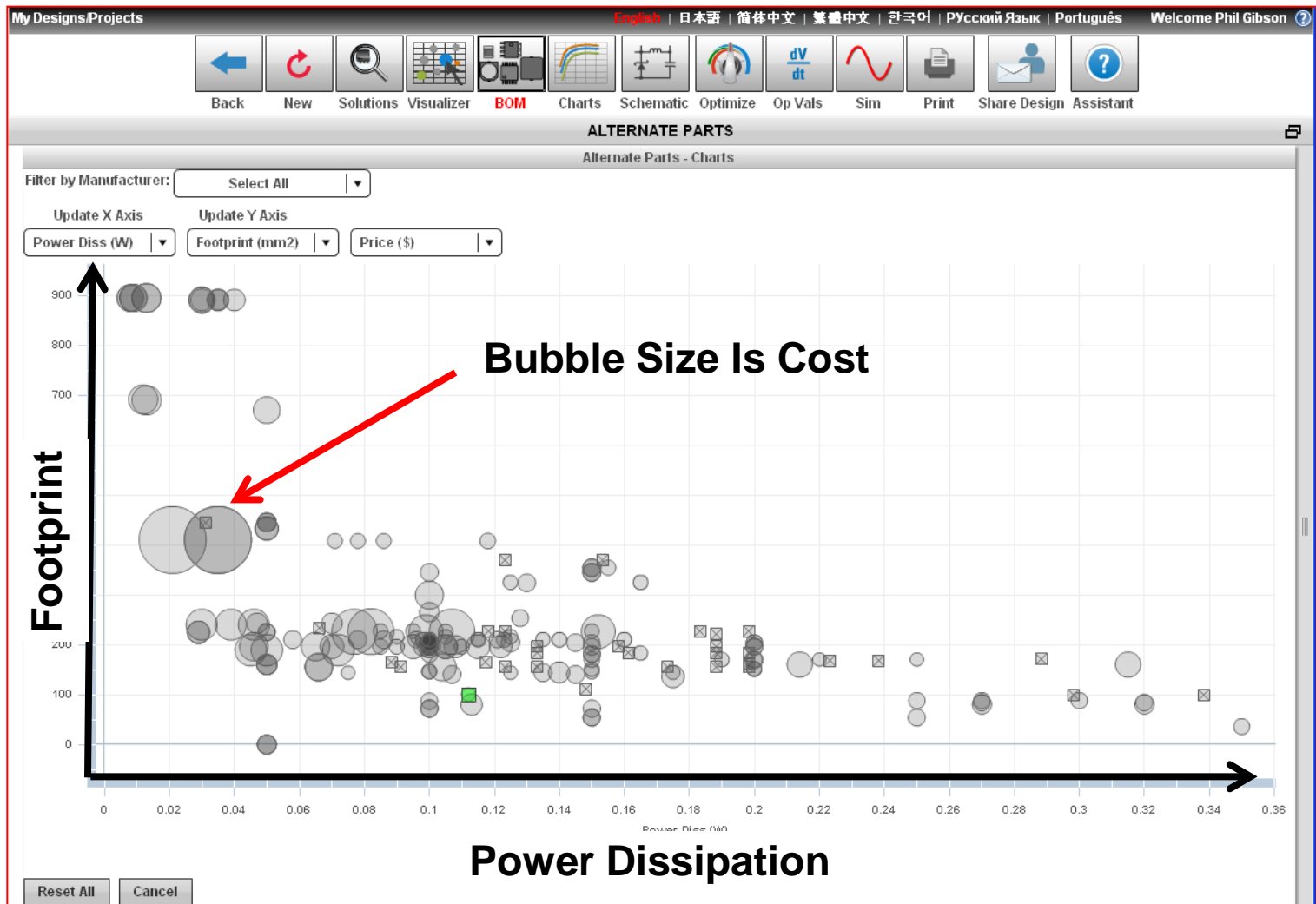


Change Perspective - Inductor

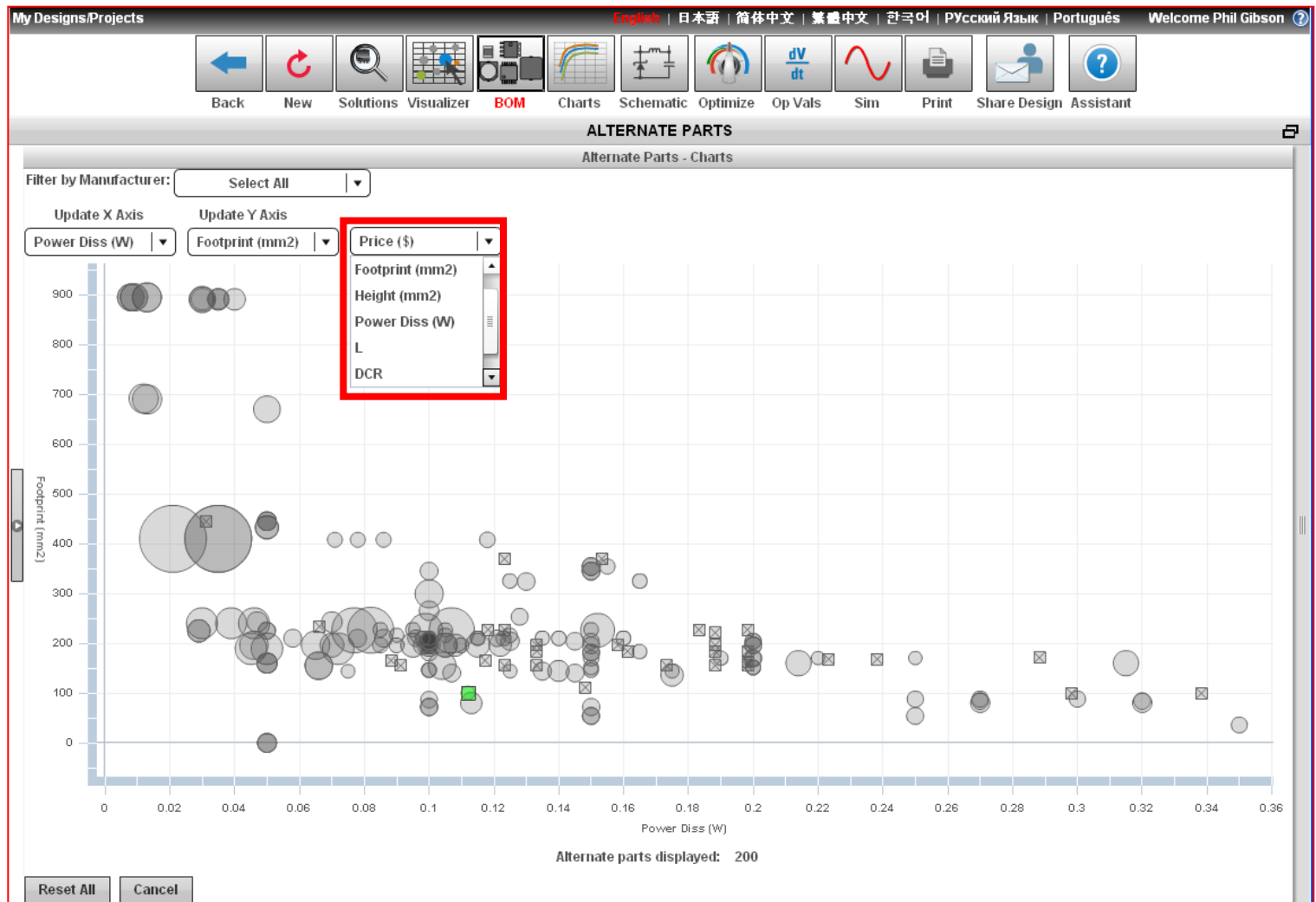

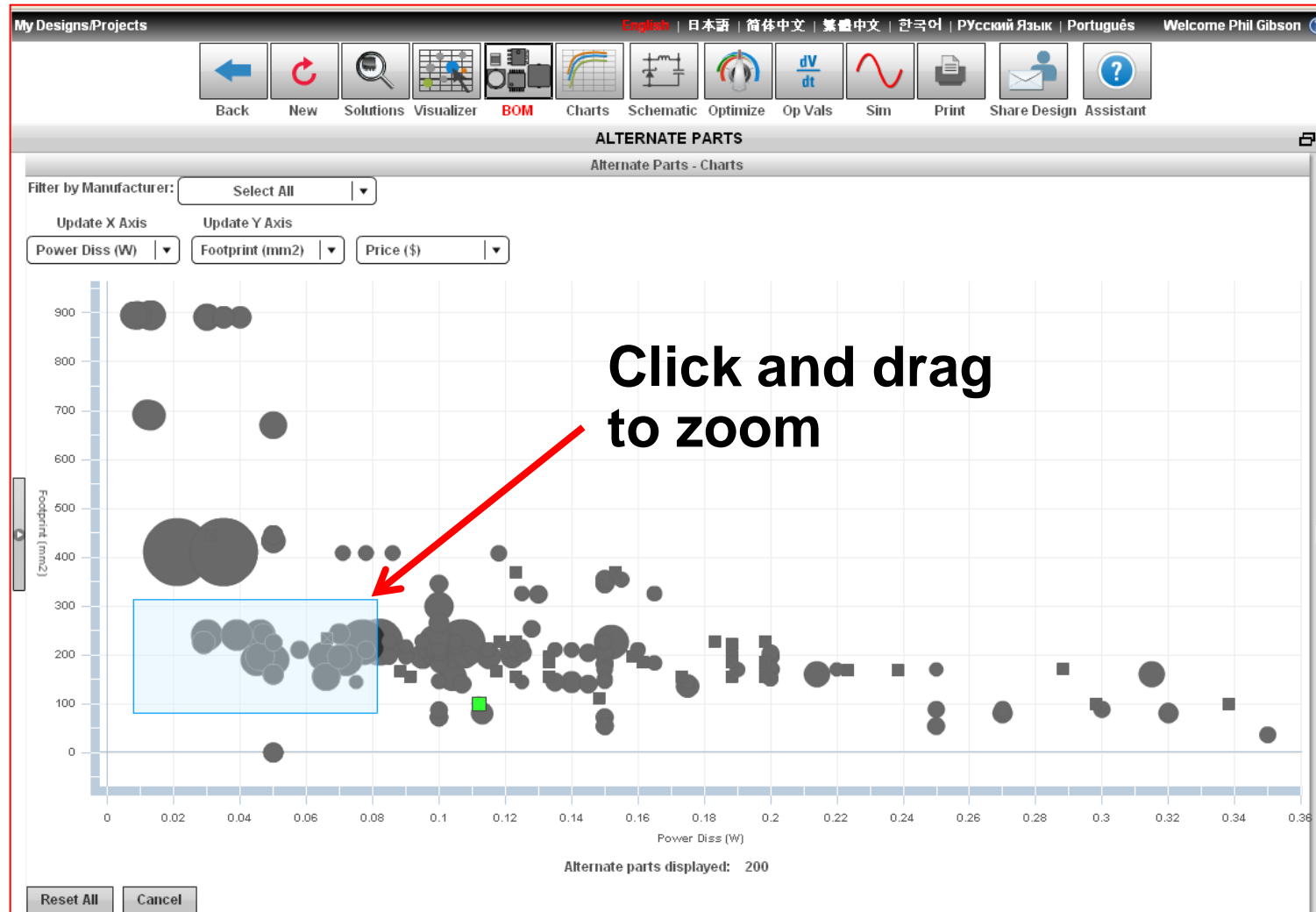Evaluate Components – Zoom to Highlight for More Detail



Evaluate Components – Zoom to Highlight

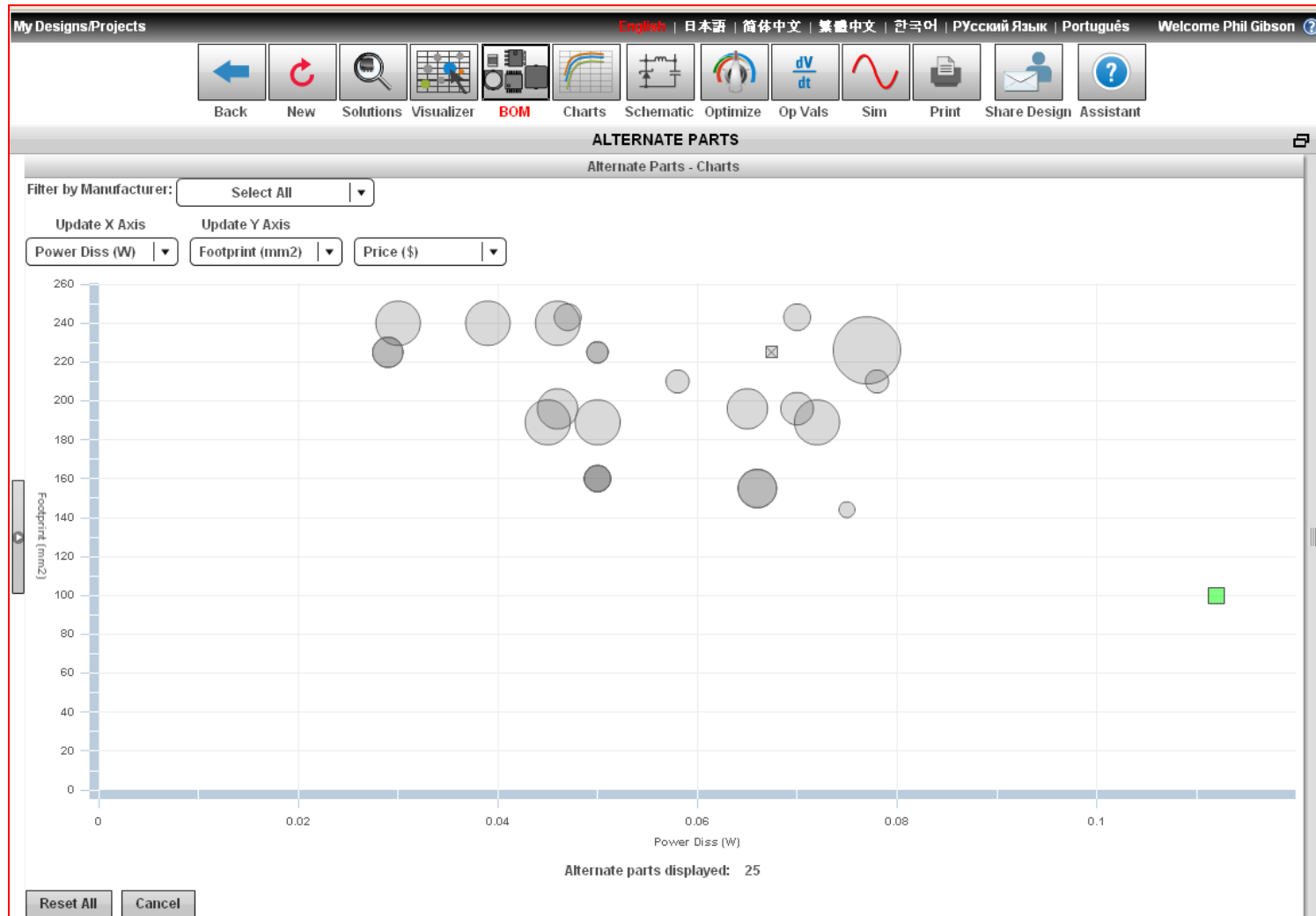

Select New Component

Filtered list
based on
zoom box

Click to select
a component

Or create a
custom
component

My Designs/Projects

English | 日本語 | 简体中文 | 繁體中文 | 한국어 | Русский Язык | Português | Welcome Phil Gibson

Back New Solutions Visualizer **BOM** Charts Schematic Optimize Op Vals Sin Print Share Design Assistant

ALTERNATE PARTS

Summary information for selected Component Summary information for selected Component L1:

Manuf	Part Number	L (H)	DCR (Ohm)	IDC (A)	Price	Qty Avail	Foot Print	Height	Power Diss	Top View
Bourns	SRU8043-6R8Y	6.8u	0.022	3.8	\$0.36	0	100	4.3	0.112	

LIMITS

	L (H)	DCR (Ohm)	IDC (A)
Upperbound	12.82u	0.083	68.57
Lowerbound	6.409u	100u	3.429
Target	6.409u	8.25m	3.429

Select an alternate part for Component L1:

Edit	Manuf	Part Number	L (H)	DCR (Ohm)	IDC (A)	Price	Qty Avail	Foot Print	Height	Power Diss	Foot Print
Select	Bourns	SRU8043-6R8Y	6.8u	0.022	3.8	\$0.36	0	100	4.3	0.112	
Select	Pulse Engineering	P0751.103NLT	10u	0.05	3.8	\$0.33	> 10	170	5.46	0.250	
Select	Pulse Engineering	P0751.682NLT	6.8u	0.044	4.4	\$0.33	> 10	170	5.46	0.220	
Select	Bourns	SRU1038-100Y	10u	0.025	3.8	\$0.36	> 10	144	3.8	0.125	
Select	Bourns	SRU1048-8R2Y	8.2u	0.015	4.6	\$0.36	0	144	4.8	0.075	
Select	Collcraft	XAL4030-682ME	6.8u	0.07	3.6	\$0.60	> 10	36	3.1	0.350	
Select	Bourns	SRU1038-7R0Y	7u	0.035	4	\$0.40	0	144	3.8	0.175	
Select	PM3340-100MR	10u	0.033	3.5	\$0.46	> 10	183	11.5	0.165		

Alternate parts displayed: 200

Reset All Cancel

Create a Custom Part Cancel Reset All

NOTE: Limits Do Not Apply To Custom Parts

Hands-on Exercise:

Design Problem:	Goals:
<p>Management has requested a design using the LM22680: Create the following design: Vin: 14-22V Vout: 3.3V Iout: 2A</p>	<p>Try optimization knob settings 1 and 5 and note: Frequency Footprint BOM cost Efficiency</p>

Why Do Electrical Simulation?

Identify Problems

- Design has been configured for stable operation **BUT**
- May want to verify under dynamic conditions

Try Solutions

- Improve line/load transient response
- Minimize output voltage ripple
- Modify control loop

Visualize Results

- Interactive waveform viewer allows detailed analysis of results


Electrical Simulation

Esim page

Specify sim type

Click start to initiate sim

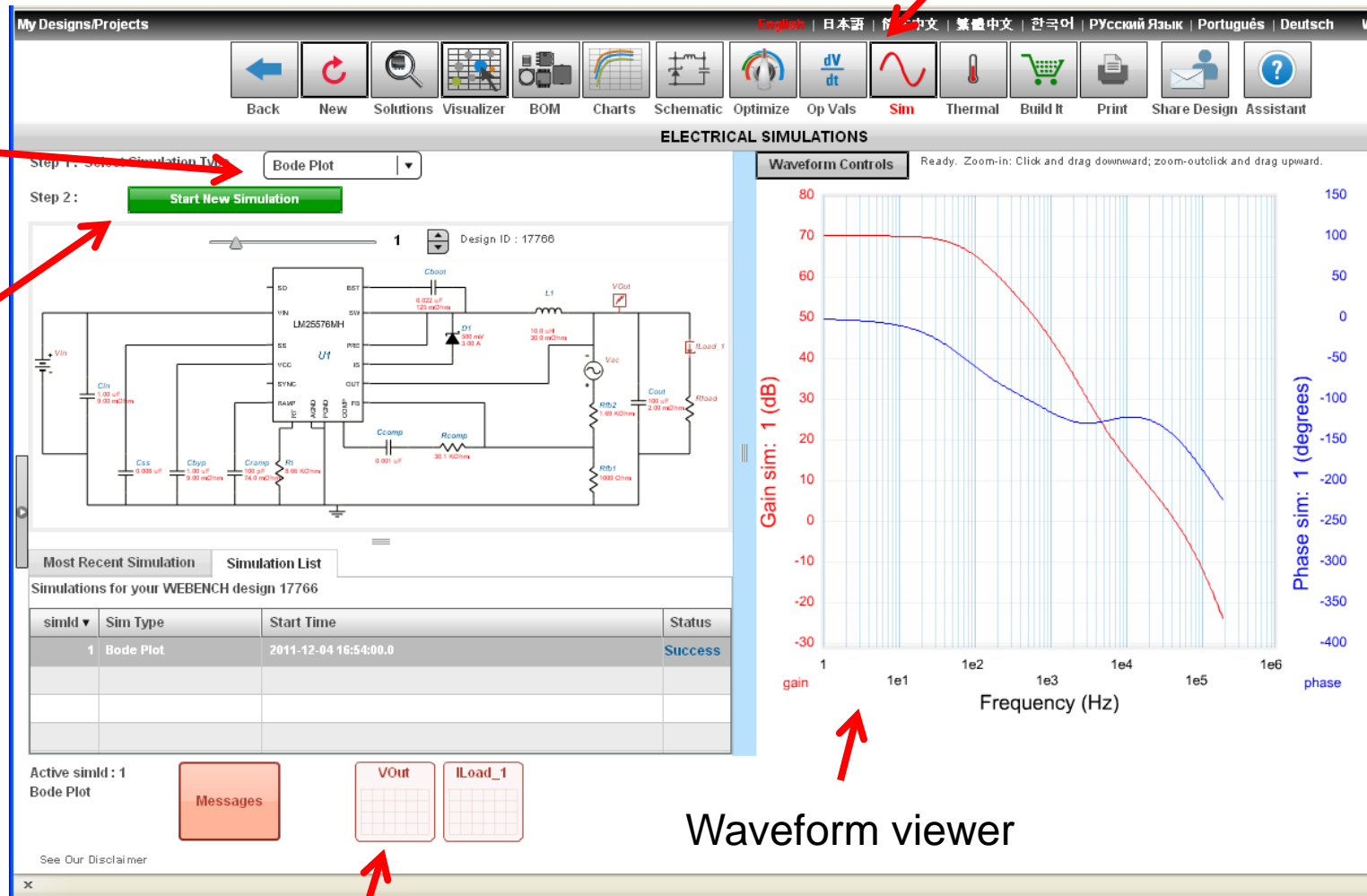- Bode Plot
- Line Transient
- Load Transient
- Startup
- Steady State




Click to view waveforms

Waveform viewer

Waveform Viewer

Click and drag down and to the right to zoom in

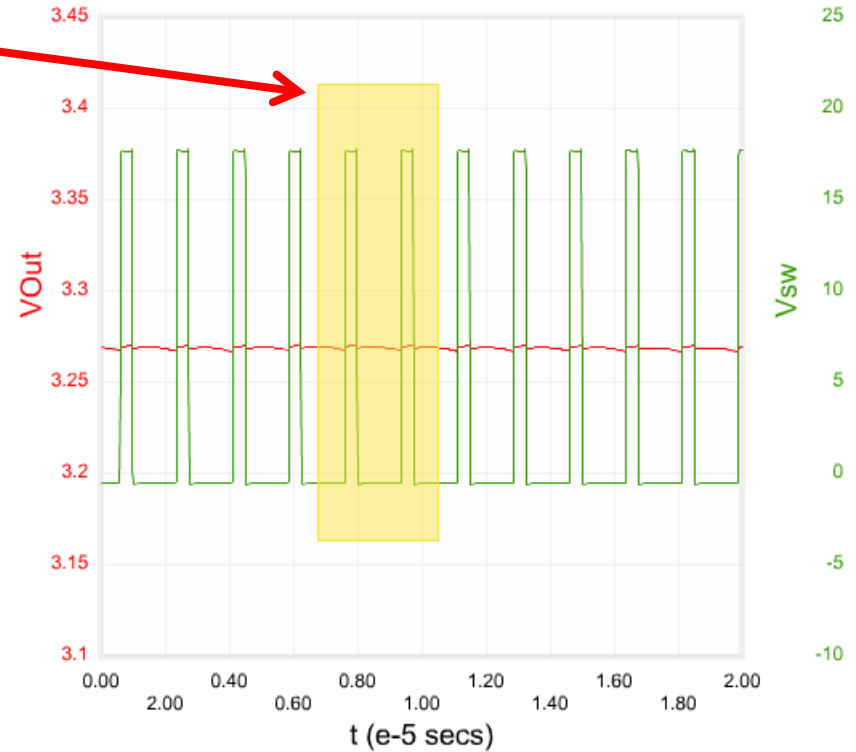Click and drag up and to the left to zoom out



Click on a tile to add a waveform




Evaluate Transient Response


- LM22680
 - Voltage mode pulse width modulation control scheme (PWM)
 - Lower part count – SIMPLE SWITCHER®
- LM25576
 - Emulated current mode (ECM)
 - Fast transient response
- Will evaluate:
 - How does ECM compare with PWM
 - Vin: 14-22V, Vout: 3.3V, Iout: 2A

Buck Schematics

LM22680 PWM

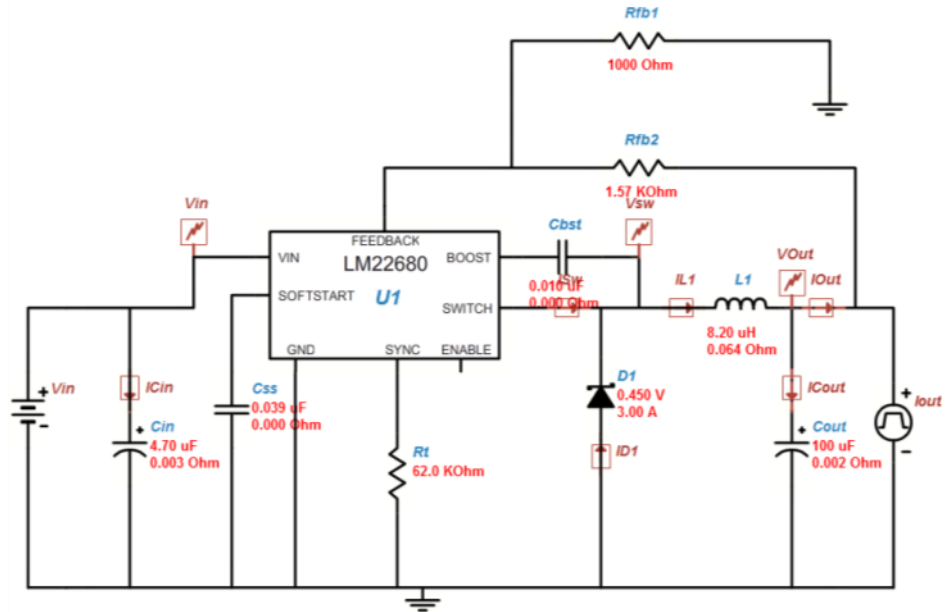


LM25576 ECM

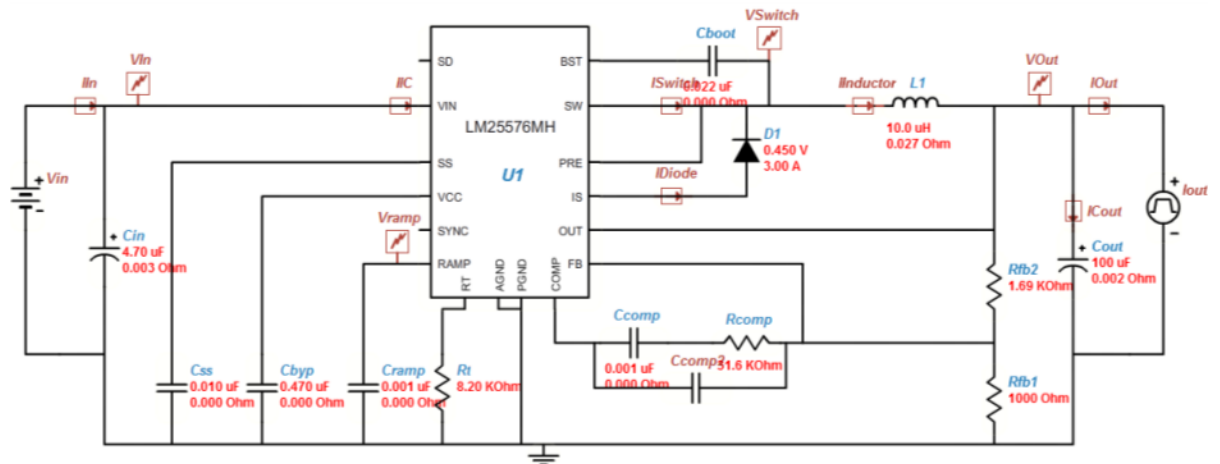


LM22680 vs. LM25576

Vout for Load Transient

- LM22680 (Pulse Width Modulated)

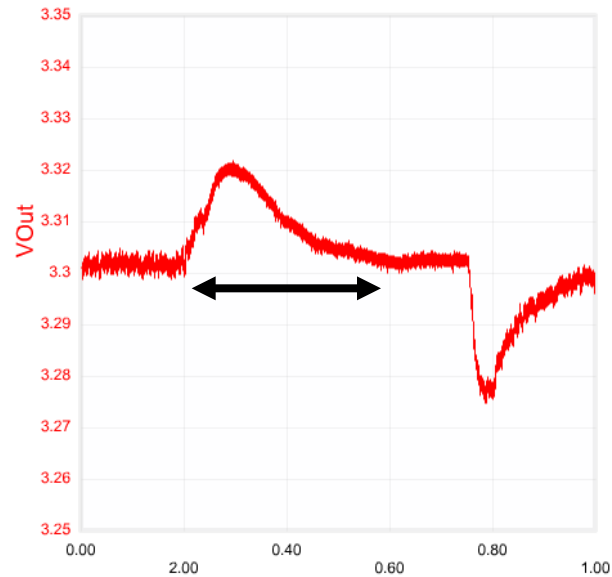

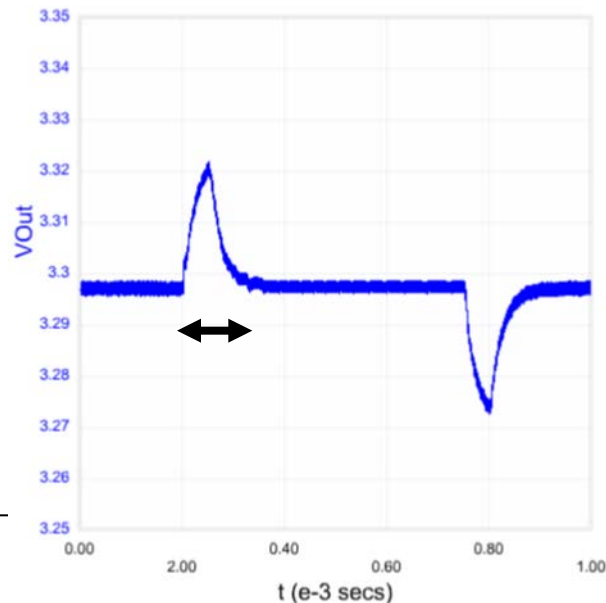
- LM25576 (Emulated Current Mode) has faster transient response recovery time





Load Transient:
.2 – 2A
50usec rise/fall time

Overlay Simulations

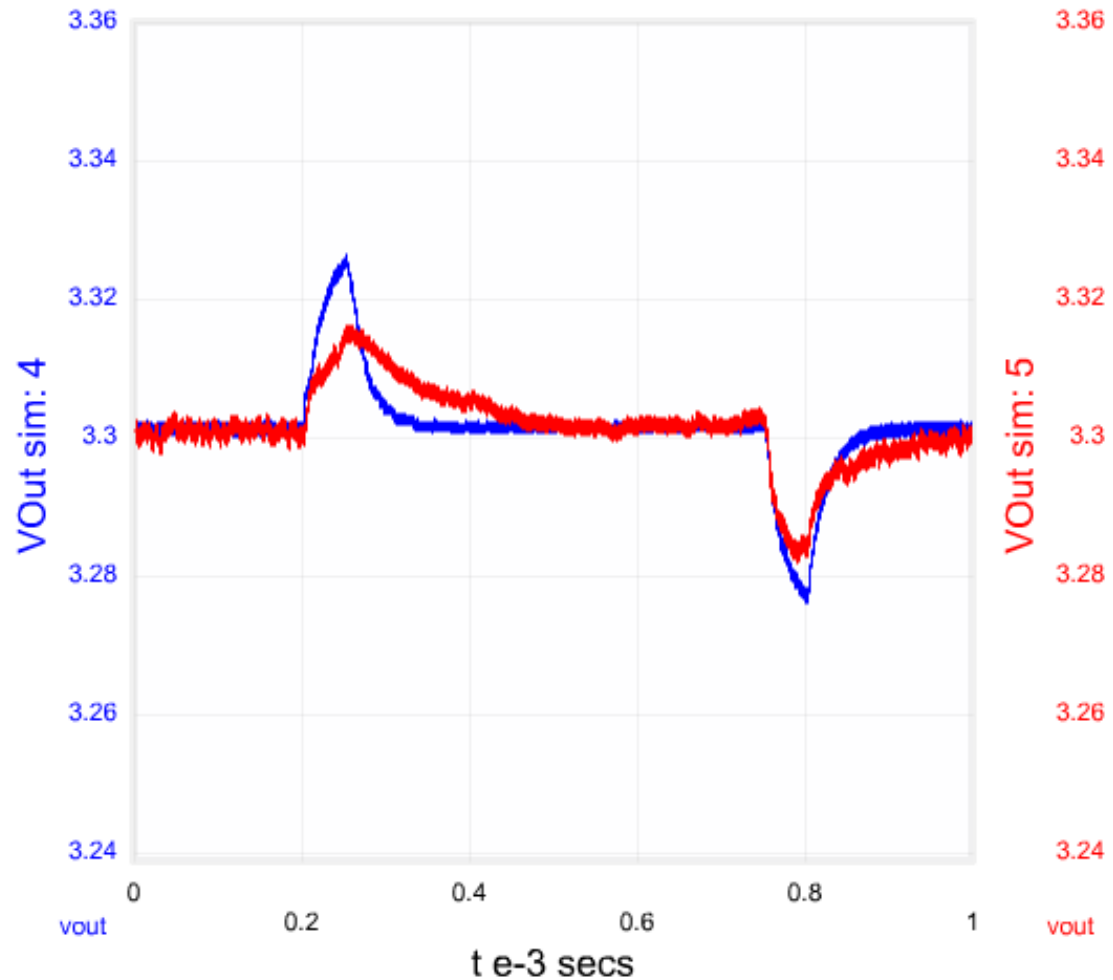
- Red: LM22680 (Pulse Width Modulated)
- Blue: LM25576 (Emulated Current Mode) has faster transient response recovery time



WEBENCH® Bode Plot Verification

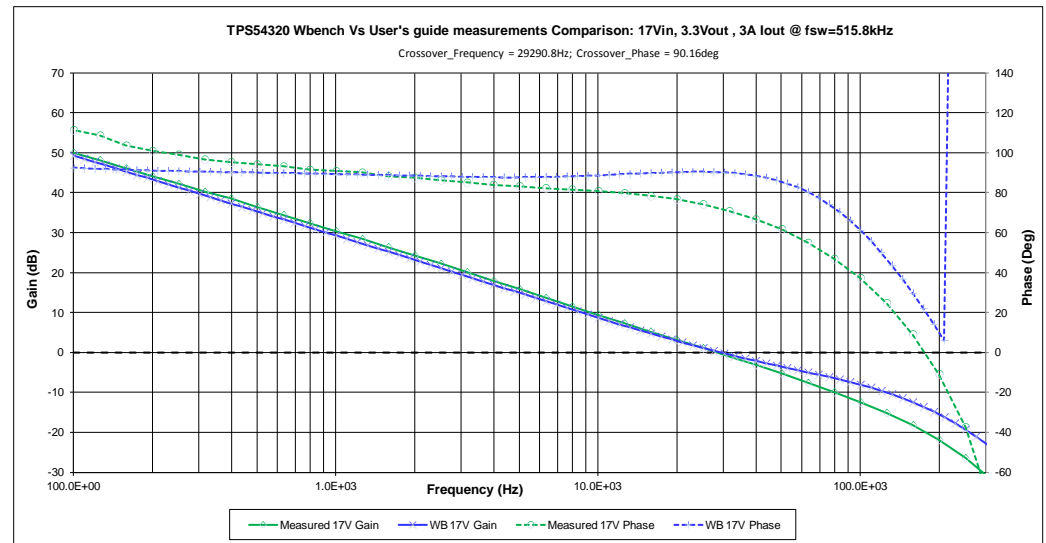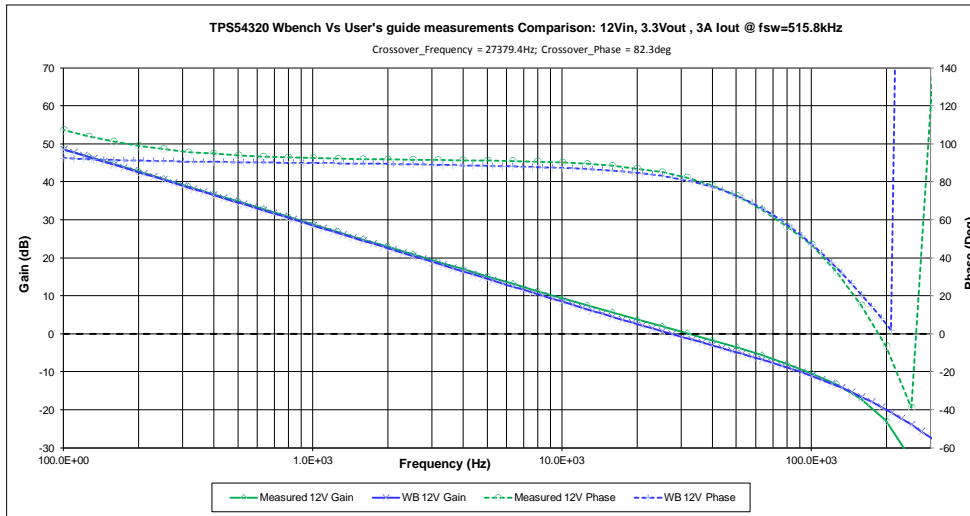

WEBENCH[®] Bode Plot Verification

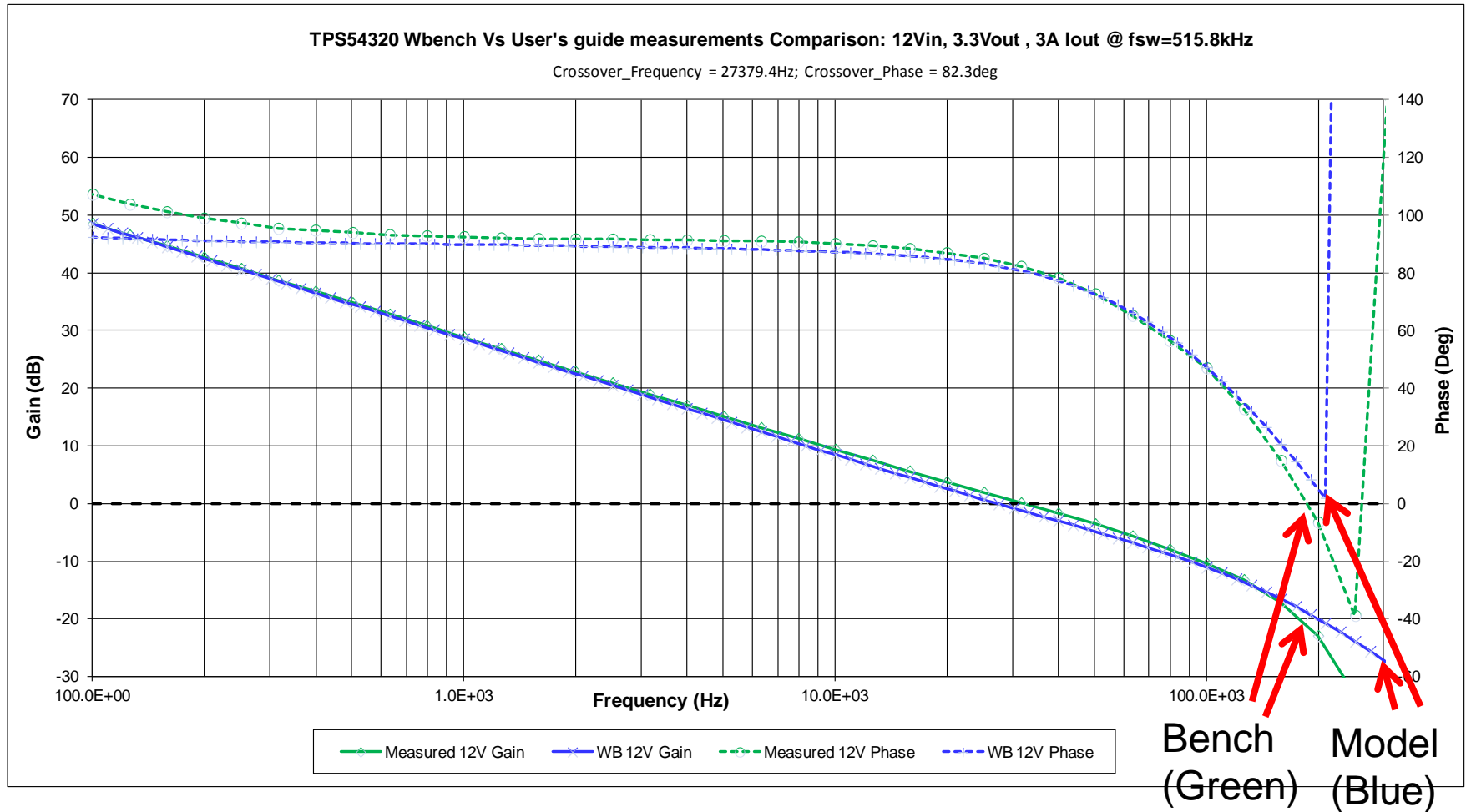

Hands-on Exercise:

Design Problem:	Goals:
<p>Management has requested to check the load transient behavior of the following design:</p> <ul style="list-style-type: none">Vin: 14-22VVout: 3.3VIout: 1AOptimization 3LM5010	<p>Run a load transient simulation and note the overshoot and recovery time.</p>

Why Do Thermal Simulation?

Identify Problems

- Co-heating of parts not accounted for with ThetaJA

Try Solutions

- Change copper thickness, airflow, ambient temperature, voltage, current

Visualize Results



- Color temperature plot across the board
- Adjustable scaling

Why Do Thermal Simulation?

- Identify and solve thermal issues
 - Co-heating of adjacent parts not taken into account with thetaJA
- Different ways to solve thermal problems:
 - Heat sink
 - Fan
 - Copper area/thickness
- Thermal simulation factors
 - Model Types:
 - Physical geometry/materials modeled for regulator
 - Lumped cuboid models for passive components
 - Board modeled as a separate part, with traces modeled explicitly
 - Simulation accuracy
 - 3D conduction
 - Radiation
 - Convection

WebTHERM® – Board Layout

Thermal Sim Page

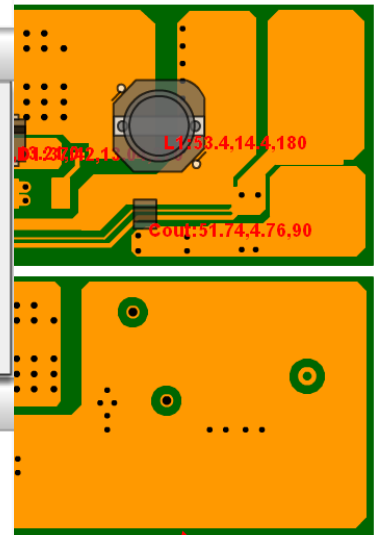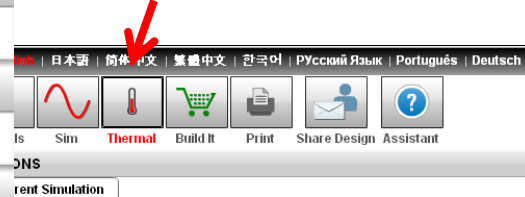

PC Board

Thermal Sim Parameters

Operating Condition

Vin: 22 Iout: 2

Ambient Temperature

On Bottom: 30 °C On Top: 30 °C

Board Condition

Copper Weight: 2 OZ.(0.07112 mm) Board Orientation: Component Side Up

Air Flow

Direction: Velocity: Use Fan None 0 LFM LMM

Edge Temperatures

Edge 1 ☒ Insulated OR 30 °C

Edge 4 ☒ Insulated OR 30 °C


Edge 2 ☒ Insulated OR 30 °C

Edge 3 ☒ Insulated OR 30 °C


- Inputs:
- Input voltage
 - Current
 - Top and bottom ambient temperature
 - Copper thickness
 - Airflow
 - Board orientation

WebTHERM[®] Results

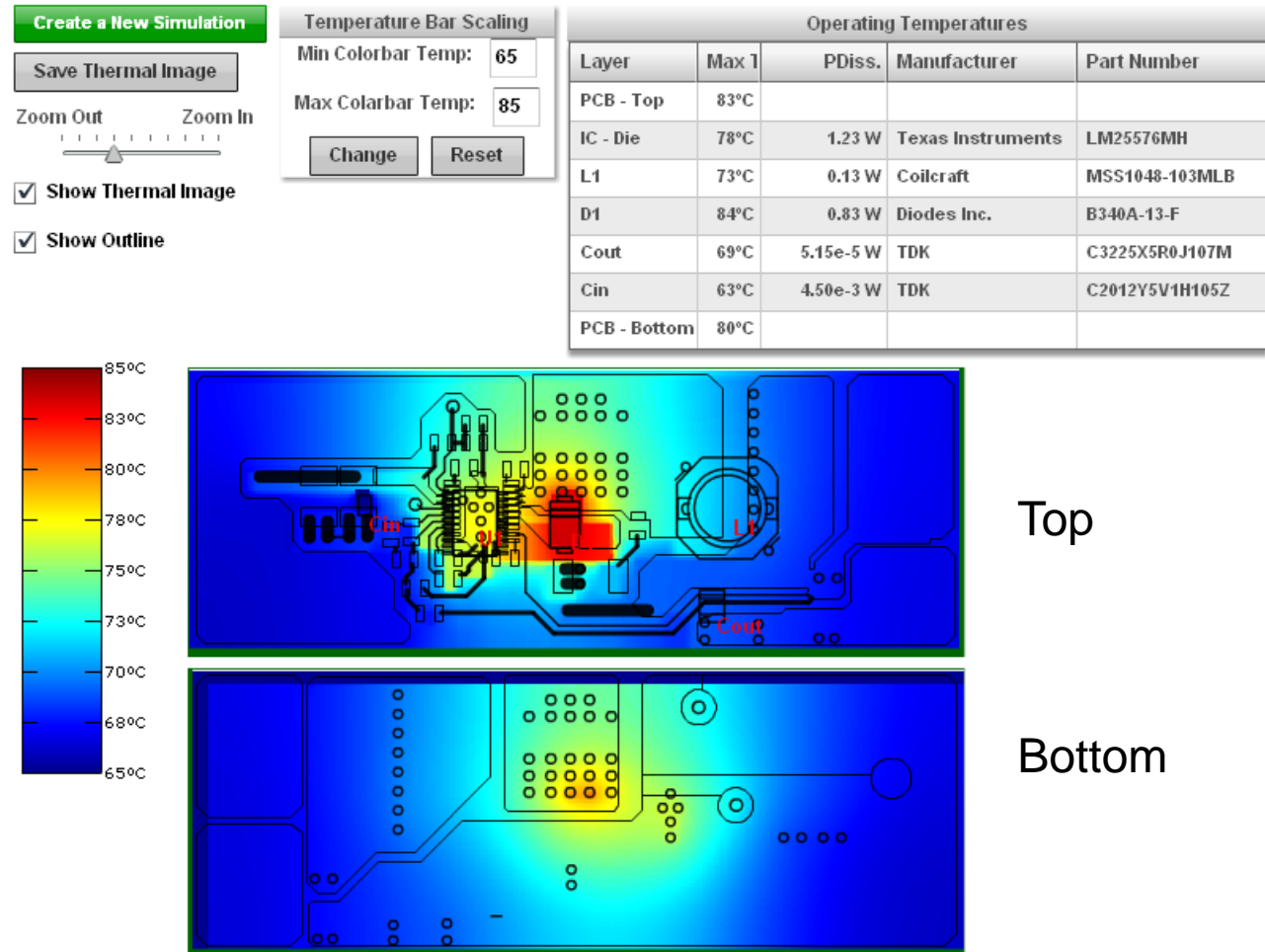
- View interactions between components
- Diode and IC both generate heat
- Effect of backside copper and vias



LM3150 Controller

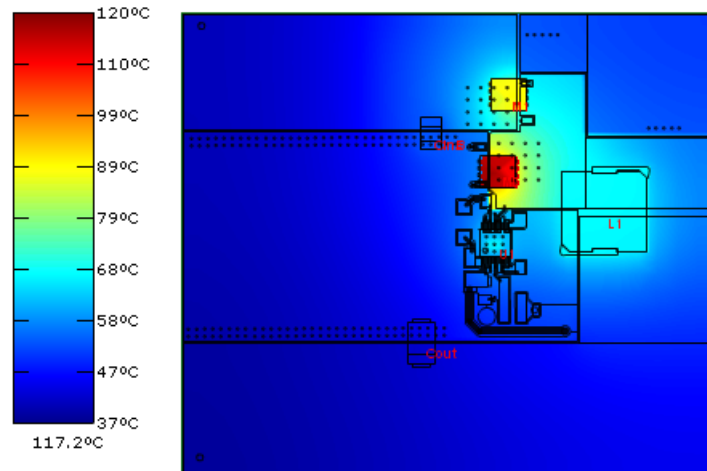

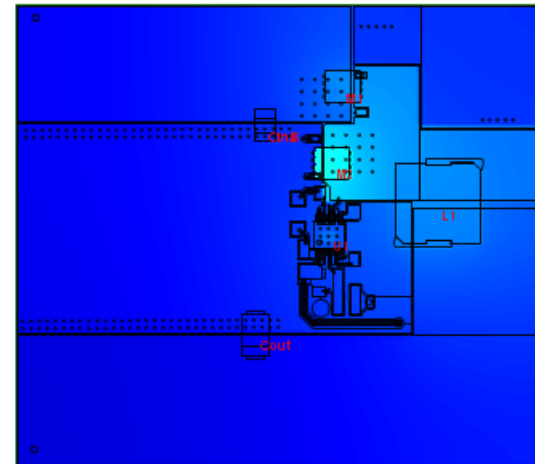
.5oz copper thickness
Low side FET is 117C




4oz copper thickness
Low side FET is 68C

Vin: 14-22V
Vout: 3.3V
Iout: 6A

WebTHERM® Solutions

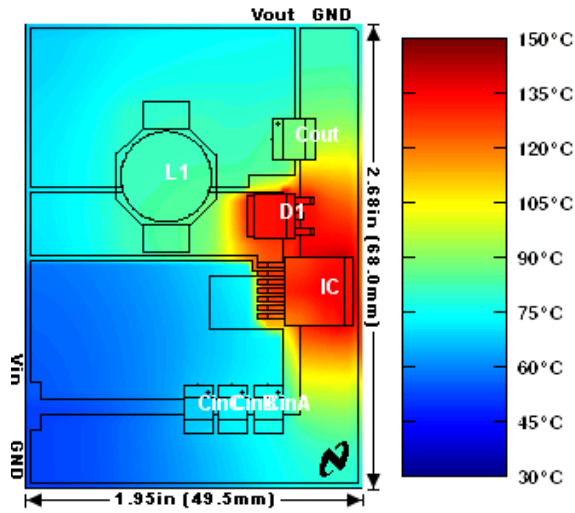


Use a Fan

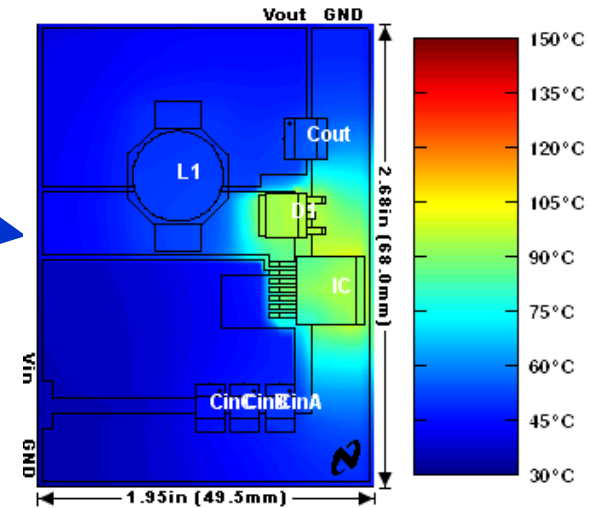

- No airflow
- Diode: 134°C
- IC: 146°C

Or add a Heat Sink

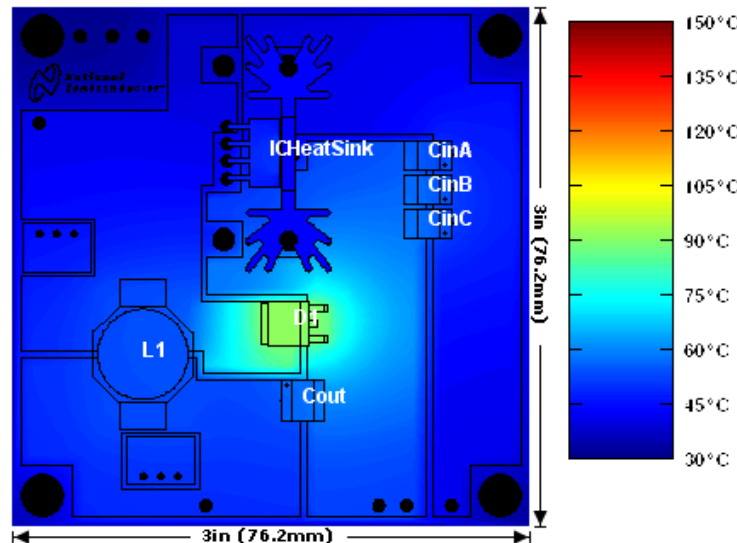

Design Specs:
 Vin: 20-22V
 Vout: 5V
 Iout: 5A

- No airflow
- Heat sink
- Diode: 91°C
- IC: 52°C

Hands-on Exercise:

Design Problem:	Goals:
<p>Management has requested to create the following design:</p> <ul style="list-style-type: none">Vin: 14-22VVout: 3.3VIout: 9AOptimization 1 (small footprint)LM3150Temperature must be below 70C	<p>Run thermal simulations to determine what can be done to bring the design into spec.</p>

Build It®

Build It Page



My Designs/Projects

English | 日本語 | 简体中文 | 繁體中文 | 한국어 | Русский язык | Português | Deutsch | Welcome Jeff Perry

Back New Solutions Visualizer BOM Charts Schematic Optimize Op Vals Sim Thermal **Build It** Print Share Design Assistant

Export to: ☒ Excel Kit Quantity: 1 Do you have a coupon? **Grand Total: \$ 40.84** **Order**

Electrical Components

Part Number	Manufacturer	Component	Qty Avail	Qty Req per Kit	Order Minimum	Qty Ordered	Prototype Price*	Total	Top View	Edit
CRCW080530K1FKEA	Vishay-Dale	Rcomp	> 10	1	10	10	\$ 0.09	\$ 0.90		Select Alternate Part
GRM155R71E822KA...	MuRata	Css	> 10	1	10	10	\$ 0.04	\$ 0.40		Select Alternate Part
C0805C102K5RACTU	Kemet	Ccomp	> 10	1	10	10	\$ 0.08	\$ 0.80		Select Alternate Part
LM25576MH	Texas Instruments	U1	> 10	1	1	1	\$ 6.13	\$ 6.13		Select Alternate Part
C0805C223K5RACTU	Kemet	Cboot	> 10	1	10	10	\$ 0.13	\$ 1.30		Select Alternate Part
B340A-13-F	Diodes Inc.	D1	> 10	1	1	1	\$ 0.50	\$ 0.50		Select Alternate Part
C3225X5R0J107M	TDK	Cout	> 10	1	1	1	\$ 1.30	\$ 1.30		Select Alternate Part
C2012Y5V1H105Z	TDK	Cin	> 10	1	1	1	\$ 0.26	\$ 0.26		Select Alternate Part
MSS1048-103MLB	Coilcraft	L1	Free ** Sample	1	1	1	\$ 0.00	\$ 0.00		Select Alternate Part

Mechanical Components

Part Number	Manufacturer	Component	Qty Avail	Qty Req per Kit	Order Minimum	Qty Ordered	Prototype Price*	Total	Top View	Edit
1727010	Phoenix Contact	J1	> 10	1	1	1	\$ 0.91	\$ 0.91		Select Alternate Part
7693	Keystone	J2,J3	> 10	2	10	10	\$ 0.58	\$ 5.80		Select Alternate Part
LM25576BLDT	Texas Instruments	PC Board	> 10	1	1	1	\$ 18.62	\$ 18.62		Select Alternate Part

*NOTE: The pricing of the BOM in WEBENCH is for prototype quantities. You can use the pricing in WEBENCH for a relative measure of cost between components when you are optimizing your design, but you will likely get a much lower total BOM cost when you go into production at higher volumes.
This Build It Kit price does not include the minimum quantity amount or shipping cost.

* NOTE: The Coilcraft inductor free sample will be shipped separately from your main order. You will receive 2 packages for your order.

*CAUTION: The items highlighted in yellow indicate that there is not enough of that part available to fulfill the requested quantity.

Order - Evaluation Boards Samples ICs

Documentation

Product Folder View My Orders

ORDER Evaluation Boards, Samples, ICs

WEBENCH Downloads:

- Schematic File
- Board Layout File
- GERBER File

Assembly Documentation

Design Documentation



Download Altium Designer Trial

Share this design

Copy this design

Complete Power Supply Design Reporting: Automatic Generation

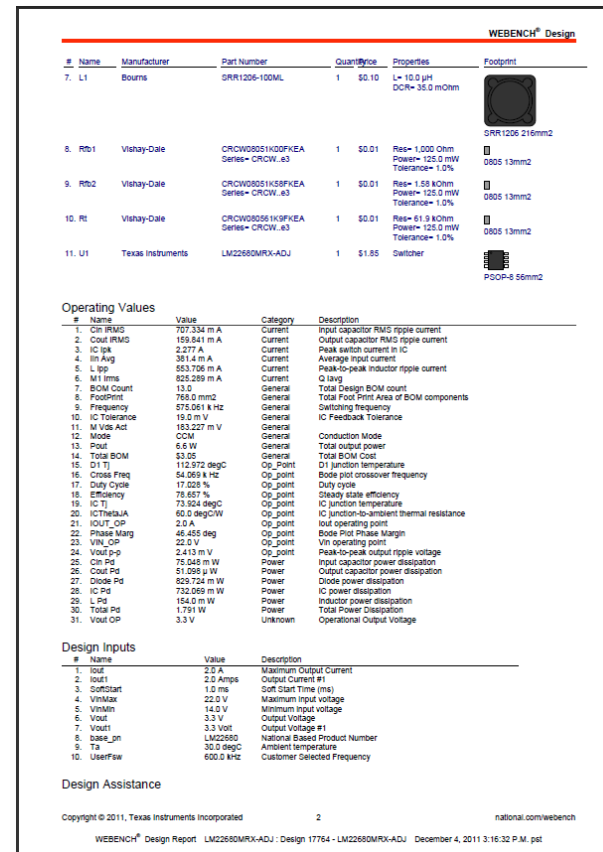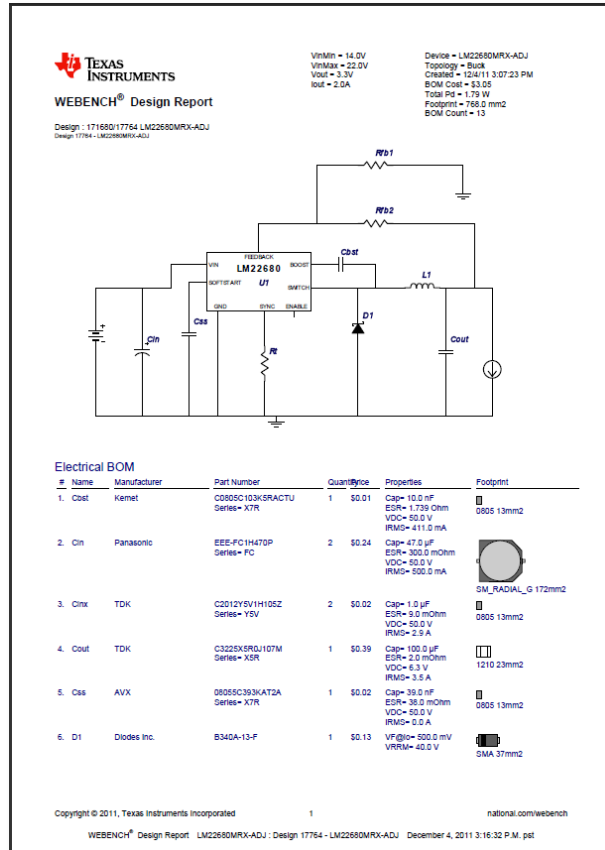Your Design From The Top: Inputs, Supplies, Schematics, BOMs





WEBENCH® Schematic Export

- TI's WEBENCH power and LED lighting design tools are the industry's leading online tools to create and optimize analog designs.
- Before: Designers create a report in PDF summarizing the WEBENCH design and manually input the schematic into the CAD tool.
- Today: With WEBENCH Schematic Export, designers can export the schematic directly to five popular CAD formats.
- Advantages:
 - Saves time
 - Reduces errors
 - Allows use of optimized WEBENCH schematics

Export WEBENCH® designs directly to CAD environment


Design Creation

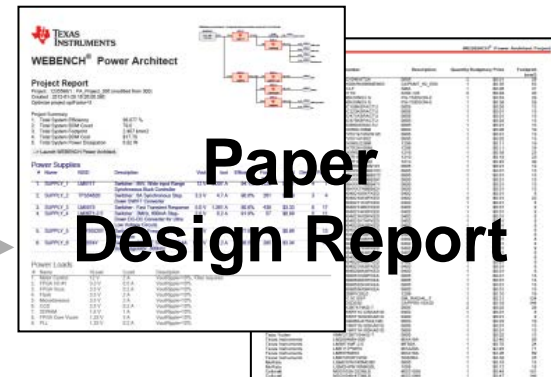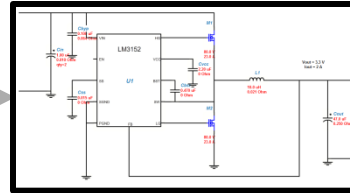

Paper Design Report

Value inputs

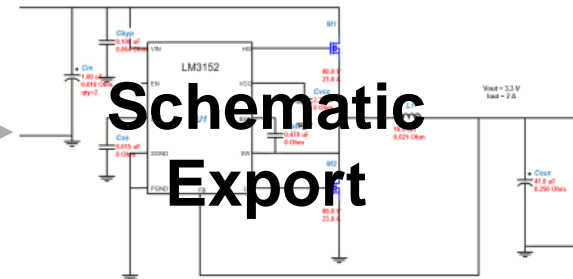- System design IP
- Component calculation
- Vendor selection
- Performance optimization
- Size optimization
- Relative pricing
- Speed/accuracy



Schematic Export


Export directly into CAD formats



Altium Designer
OrCAD Capture CIS
DxDesigner
DesignSpark
P-CAD


WEBENCH® Export Directly to CAD Tool

WEBENCH schematic

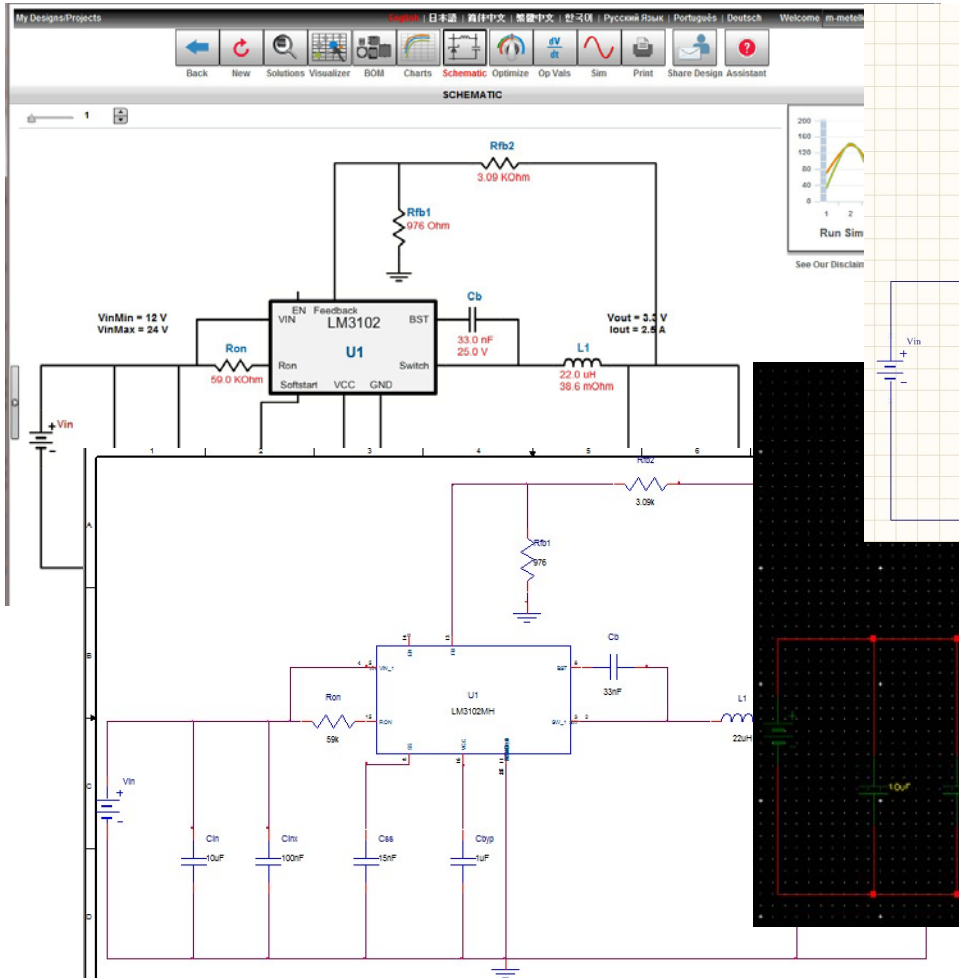


Exported schematic to Cadence OrCAD

Exported schematic to Altium Designer

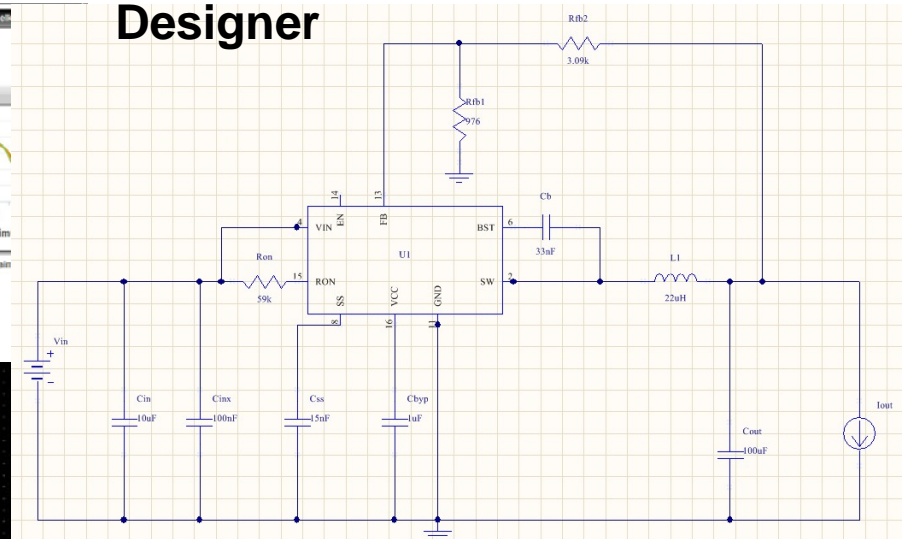

Exported schematic to Mentor Graphics DxDesigner

The WEBENCH[®] Tool Suite

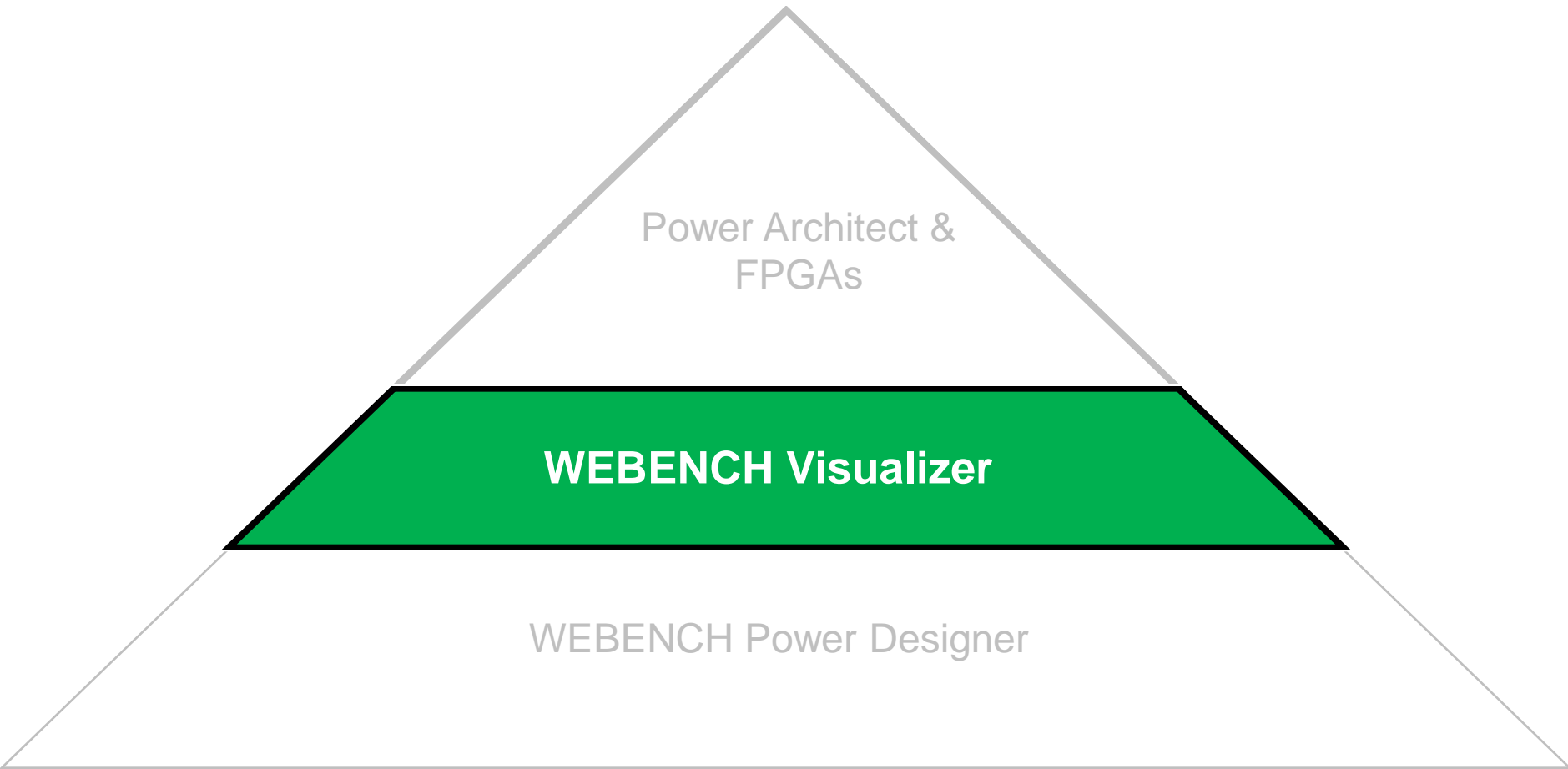


WEBENCH® Visualizer- Calculates 65 Designs in 10 Seconds




Calculated BOM Footprint, BOM Cost and Efficiency

Footprint vs Cost vs Efficiency

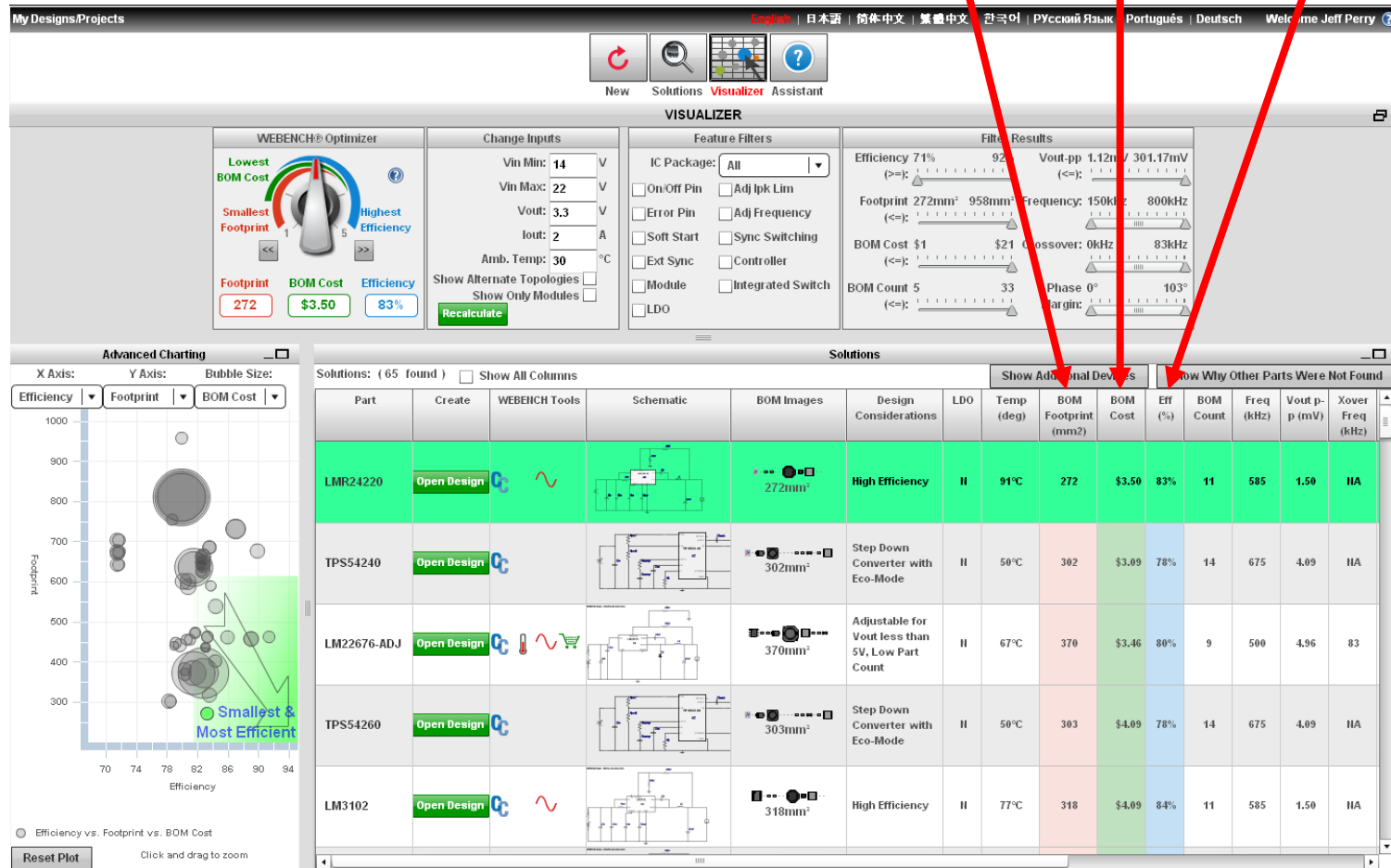

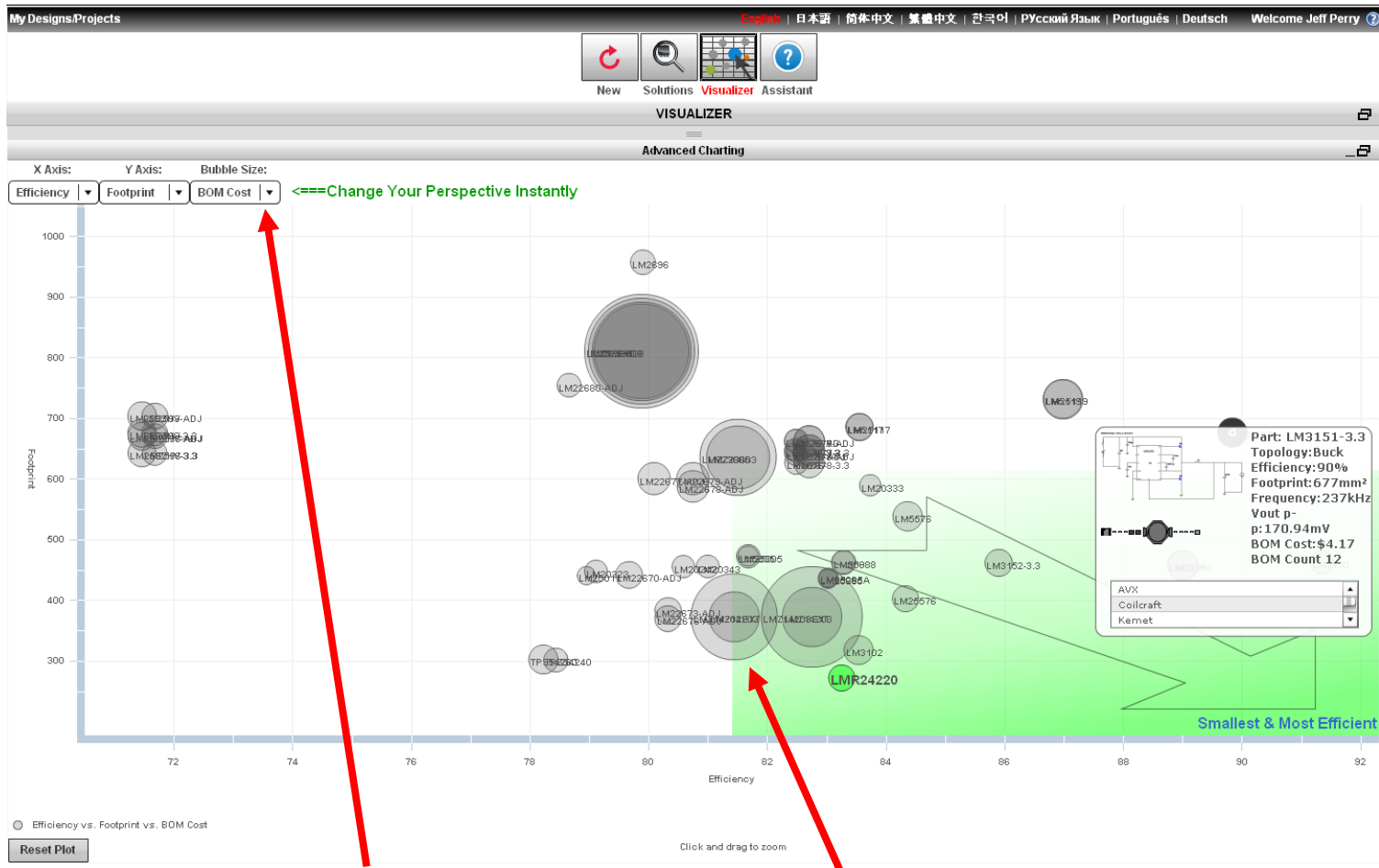Graphical Plot Gives at a Glance Trade-offs



Click on square to resize the plot to full screen size


Hover to see details

Click and drag to zoom

Change plot parameters

Bubble Size = BOM Price

Why Are the Solutions Different?

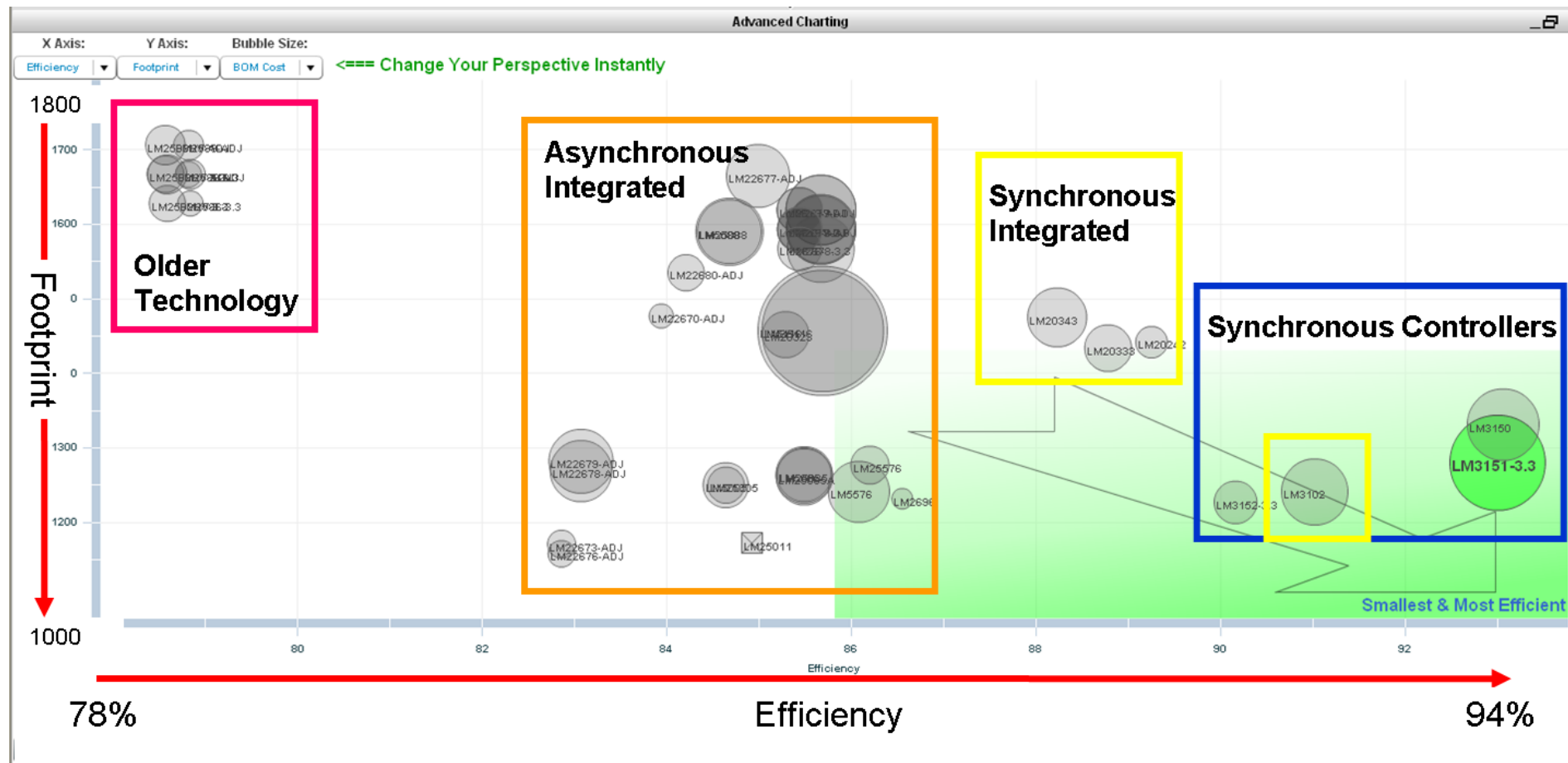

Give The Engineers What They Want: Best Efficiency, Footprint and BOM Cost


Results from example:

Filter: Integrated Switch


Vin = 14V to 22V

Vout = 3.3V


Iout = 2.0A

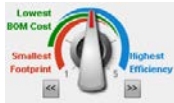

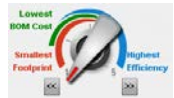- Default Setting: LM25005, 83%, 416mm², \$2.13



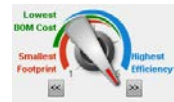- **Smallest Footprint:** LMR24220, 78%, **218mm²**, \$2.47



- **Highest Efficiency:** LM26003, **91%**, 1357mm², \$4.84

- Hint:

At each setting sort first for the most relevant parameter, then look for best compromise on the others

Hands-on Exercise:

Design Problem:	Goals:
<p>Take the previous design requirements and see if you can find a better solution than the LM22680:</p> <p>Vin: 14-22V Vout: 3.3V Iout: 2A</p>	<p>What is the system with the:</p> <ul style="list-style-type: none">Smallest footprintHighest efficiencyLowest cost <p>Note the device used and the value of all 3 factors for each design</p>

WEBENCH® Power Designer



End-to-end design solutions
Online selection, simulation and prototyping
Dynamic design optimization based on size, cost and efficiency




WEBENCH Visualizer

View dozens of designs at a time to get the best solution for a single power supply
Each design optimized for efficiency, cost and size



WEBENCH Power Architect

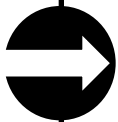System level designs for complex multiple load applications
Provides different rail architectures
Each system optimized for efficiency, cost and size



WEBENCH Design Tools save you time

Thank You!

Try WEBENCH® Tools yourself:

<http://webench.ti.com>

WEBENCH® Tool Industry Awards

- 2012 Design News Golden Mousetrap Award
 - WEBENCH System Power Architect
- 2011 EDN “Innovation of the Year”
 - WEBENCH FPGA Power Architect
- 2010 Electronic Design “Year’s Best - Power”
 - WEBENCH LED Architect
- 2010 EDN “Innovation of the Year”
 - WEBENCH Visualizer
- 2009 EDN “Innovation of the Year”
 - WEBENCH Power/LED Designer
- 2008 Electronic Products “Product of the Year”
 - WEBENCH Sensor Designer
- 2006 IEC “DesignVision” Award
 - WEBENCH Designer
- 2005 EDN “Innovation of the Year”
 - WEBENCH Active Filter Designer
- 2001 EDN “Innovation of the Year”
 - WEBENCH 3.0
- 2000 Electronic Products “Product of the Year”
 - WEBENCH 1.0



For More Information:

Existing Arrow Customers: 800 777 2776

New Customers: 800 833 3557

www.arrownac.com/powermanagement